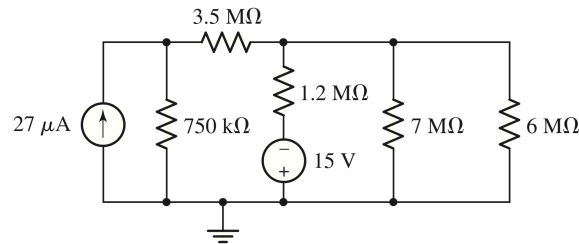



EEE 31 second semester AY2017-2018 : Homework 03

Due: 16 April 2018


- Using repeated source transformations, determine the Thevenin equivalent of the circuit below as seen by the $6\text{M}\Omega$ resistor. Use this to calculate the power delivered to the $6\text{M}\Omega$ resistor.



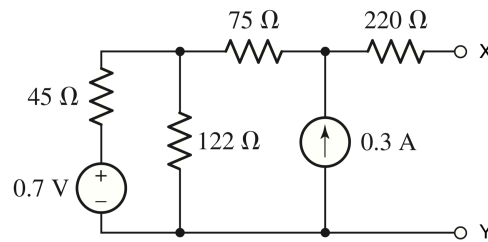
- Determine the Thevenin and Norton Equivalent of the circuit below with respect to terminals X and Y.



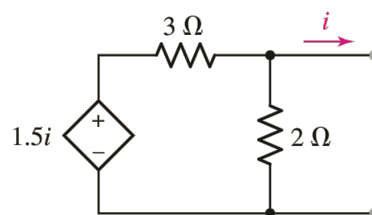- Determine the Thevenin equivalent of the circuit below with respect to the terminals shown.



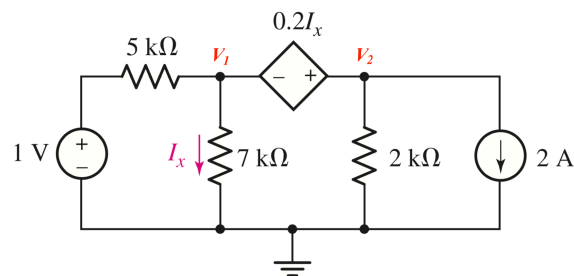- Use superposition and the node-voltage method to determine v_1 and v_2 .



- The circuit shown is a small-signal model of a bipolar transistor amplifier circuit. The sinusoidal voltage source is the input to the amplifier.
 - What value of R_L will result in maximum power being transferred to it?
 - What is the average power that will be transferred to R_L ? (Hint: Use the concept of effective voltage)

