

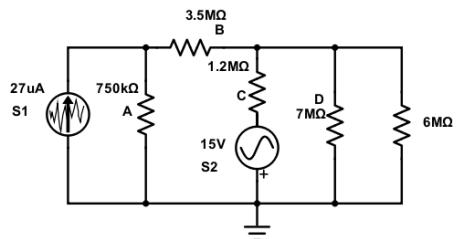


## EEE 31 HW 3 Answer Key


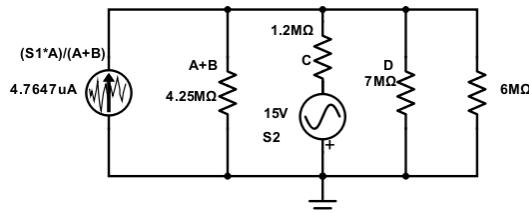
1. Follow the figure below to obtain the Thevenin equivalent circuit seen by the  $6M\Omega$  resistor.




$\Rightarrow$

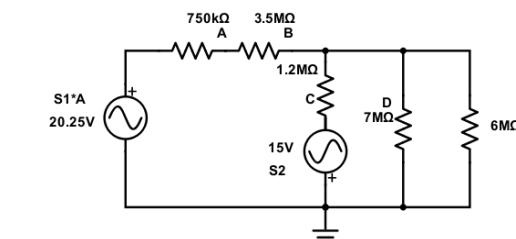

$\Rightarrow$

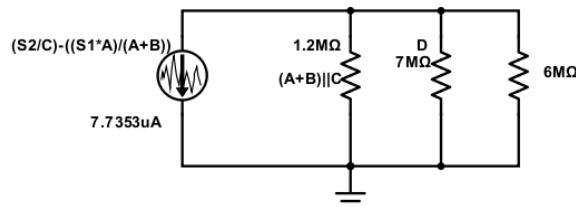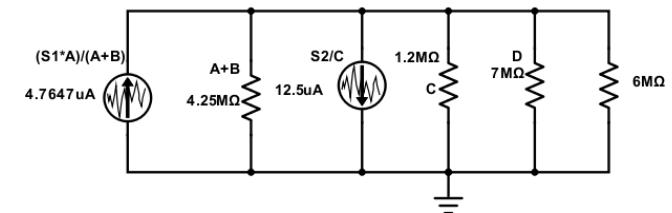


$\Rightarrow$

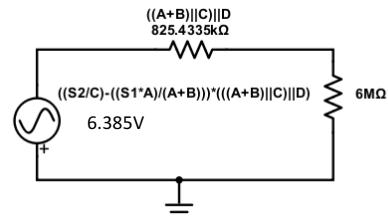

$$V_{6M\Omega} = \frac{6M\Omega}{6M\Omega + 825.4335k\Omega} (6.385V) = -5.6128V$$

$$P_{6M\Omega} = \frac{(-5.6128V)^2}{6M\Omega} = 5.2506\mu W$$

2.

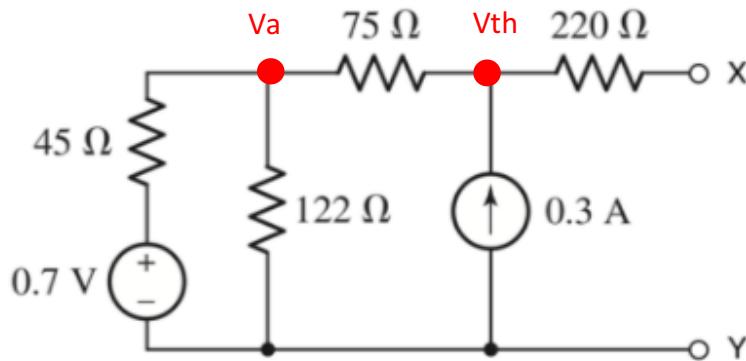

To find R<sub>th</sub>, short voltage source and open current source.

Note: You can only do this when there is no independent source in the circuit.

$$R_{th} = (45 \parallel 122) + 75 + 220 = 327.8743 \Omega$$

To find V<sub>th</sub>, find V<sub>oc</sub>.


Consider node voltage V<sub>a</sub> and V<sub>th</sub>:

$$\text{Equation 1: } \frac{V_a - 0.7V}{45\Omega} + \frac{V_a}{122\Omega} + \frac{V_a - V_{th}}{75\Omega} = 0$$


$$\text{Equation 2: } \frac{V_{th} - V_a}{75\Omega} = 0.3$$

2 equations, 2 unknowns
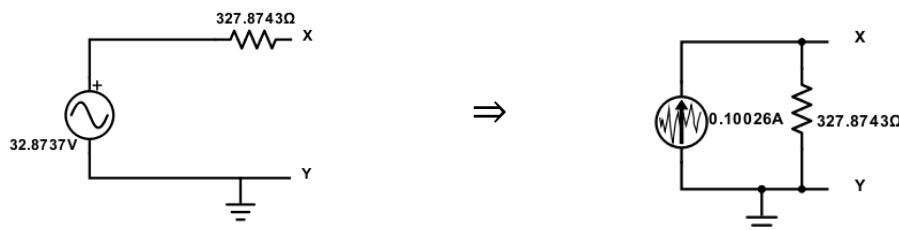
$$I_N = \frac{V_{th}}{R_{th}} = \frac{32.8737V}{327.8743\Omega} = 0.10026A$$




3.

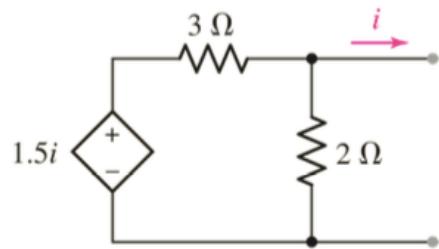


Apply Vtest, the resulting node voltage equation becomes:

$$\begin{aligned}\frac{V_t - 1.5i_t}{3\Omega} + \frac{V_t}{2\Omega} &= i_t \\ V_t \left( \frac{1}{3} + \frac{1}{2} \right) &= i_t \left( 1 - \frac{1.5}{3} \right) \\ \frac{V_t}{i_t} &= R_{th} = 0.6\Omega\end{aligned}$$

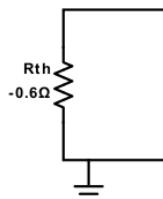No independent source is present in the circuit; therefore,  $V_{th}$  is ignored.



4.

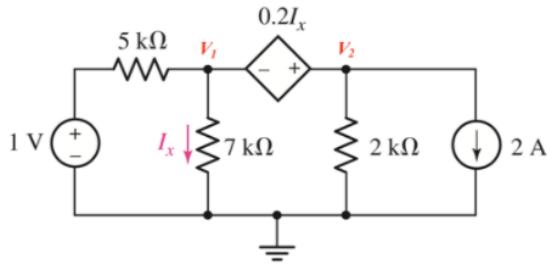

Open current source:

$$\text{Equation 1: } \frac{V_1' - 1}{5k\Omega} + \frac{V_1'}{7k\Omega} + \frac{V_2'}{2k\Omega} = 0$$

$$\text{Equation 2: } V_2' - V_1' = 0.2I_x = 0.2\left(\frac{V_1'}{7k\Omega}\right)$$

2 equations, 2 unknowns

$$V_1' = 0.2373 \text{ V}$$

$$V_2' = 0.2373 \text{ V}$$

Short voltage source:

$$\text{Equation 1: } \frac{V_1'}{5k\Omega} + \frac{V_1'}{7k\Omega} + \frac{V_2'}{2k\Omega} + 2 = 0$$

$$\text{Equation 2: } V_2' - V_1' = 0.2I_x = 0.2\left(\frac{V_1'}{7k\Omega}\right)$$

2 equations, 2 unknowns

$$V_1'' = -2372.9216 \text{ V}$$


$$V_2'' = -2372.9894 \text{ V}$$

Total:

$$V_1 = -2372.6843 \text{ V}$$

$$V_2 = -2372.7521 \text{ V}$$

5.

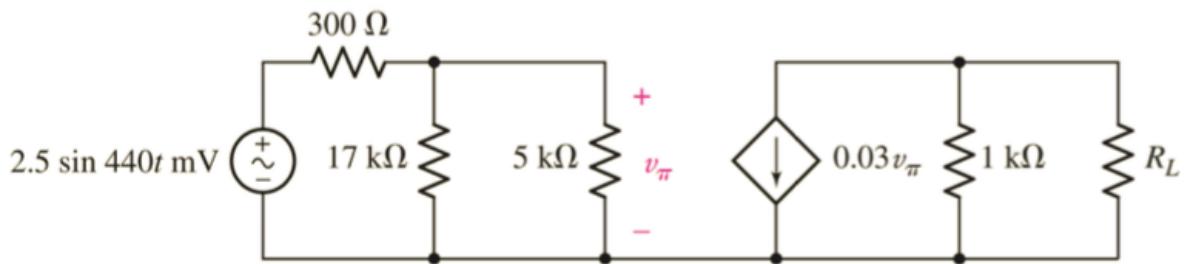

a. For maximum power transfer:

$$R_L = 1k\Omega$$

b.

$$v_{eff} = \frac{2.5mV}{\sqrt{2}}$$

$$v_{\pi} = \frac{17k\Omega || 5k\Omega}{17k\Omega || 5k\Omega + 300} (v_{eff}) = 1.6404mV$$

$$P_L = I_L^2 * R_L = \left( \frac{0.03 * 1.6404mV}{2} \right)^2 * 1k\Omega = 0.6055uW$$