

EEE 31 Problem Set 1  
 Due: December 12, 2011 (10am)

1. Find the total current supplied by the source and the power dissipated in the  $5\Omega$  resistor in the circuit given in Fig. 1.1.

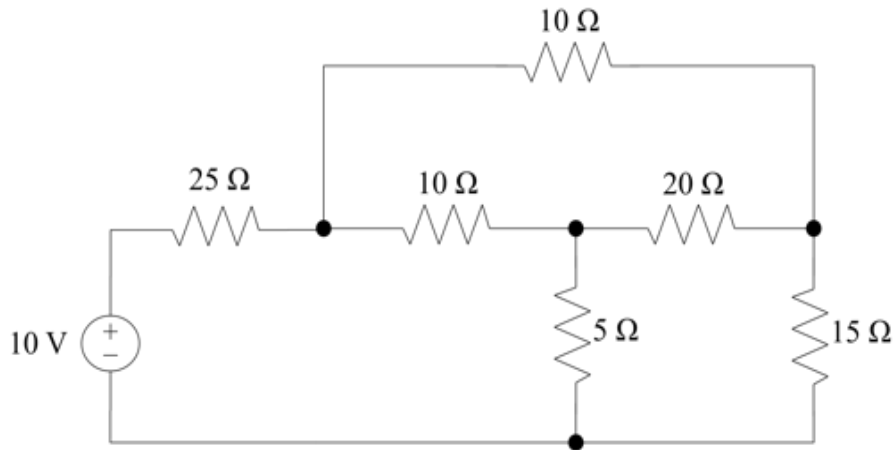


Figure 1.1. Resistor Network with 10V supply

2. Consider the network given below. Determine the equivalent resistance seen across a-b if  $R_1=10\Omega$  and the circuit element A is defined by  $v=i^2$ . Show your answer in graphical form.

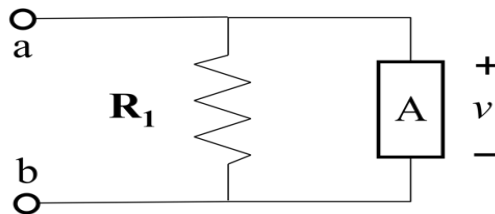


Figure 1.2. A network with linear and nonlinear elements

3. Use current and voltage division to help obtain an expression for  $v_5$ .

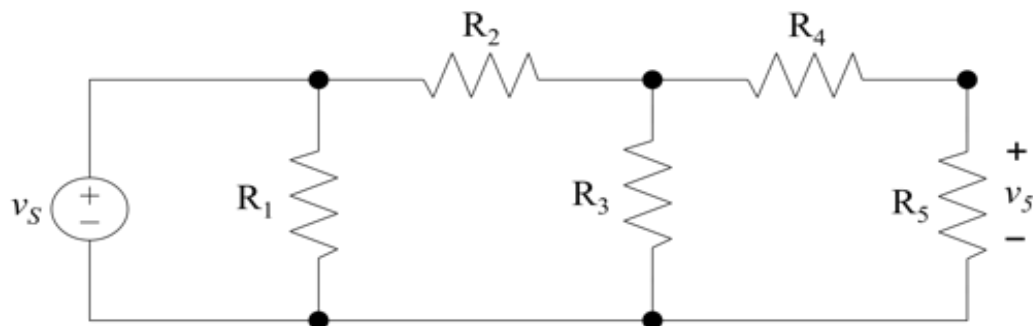


Figure 1.3. A resistive circuit

4. Compute the value of  $R$  if  $R_{eq}=9\Omega$ .

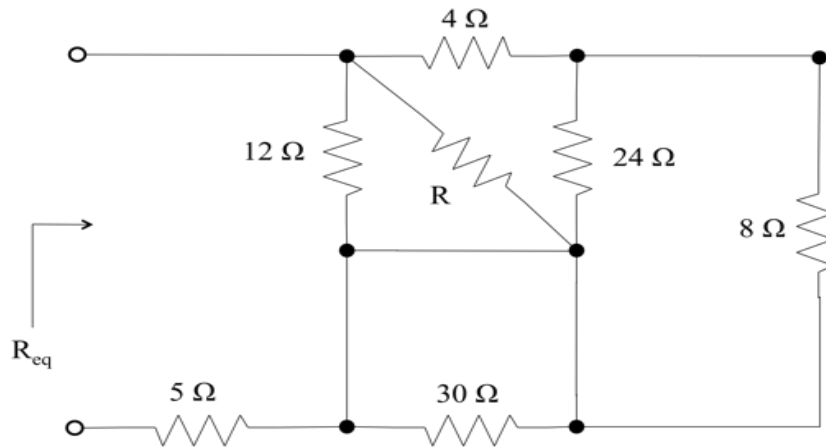


Figure 1.4. Solving for  $R$

5. Determine the resistance  $R$  and the power received/supplied by each element if the voltage across the  $0.5\text{ A}$  source is  $2\text{ V}$ .

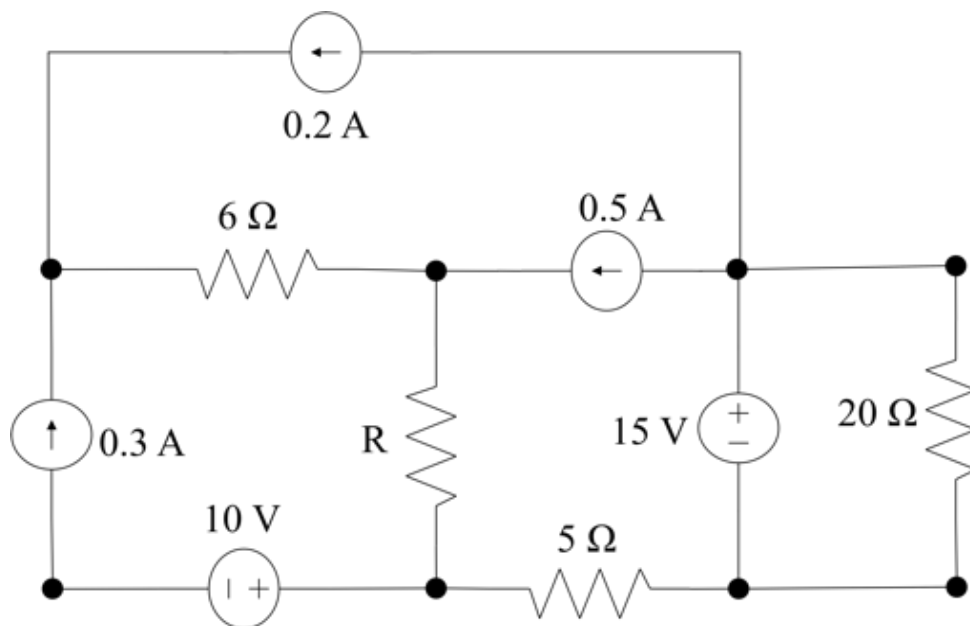


Figure 1.5. Solving for  $R$  and power