

EEE 31 Problem Set 1

Due: 23 January 2013, in class, at the start of the class

- The terminal voltage and terminal current were measured on the device shown in Fig. 1(a), and the values of v and i are plotted in Fig. 1(b).

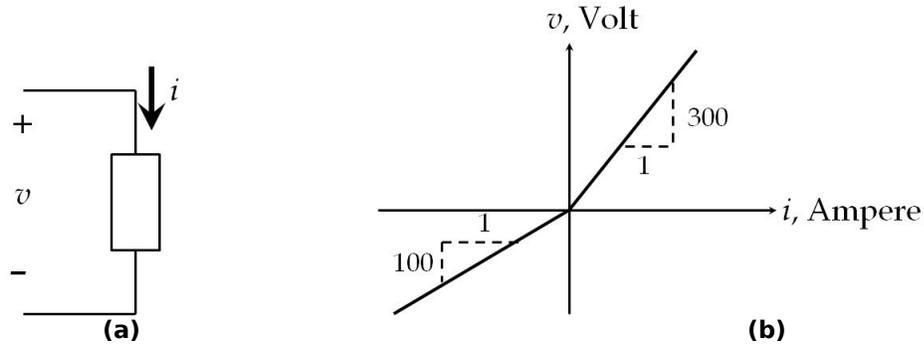


Figure 1. (a) Device and (b) its voltage-current plot

- The voltage shown in Fig. 2 is applied to the device. Sketch the current versus time plot for $0 \leq t \leq 4$ s.

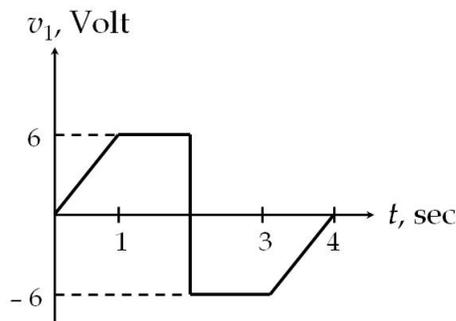


Figure 2. Voltage applied to the device in Fig. 1

- Sketch the power versus time plot for $0 \leq t \leq 4$ s.
 - Calculate the energy absorbed by the device over the time interval $0 \leq t \leq 4$ s.
- For the given circuit in Fig. 3, the sources are supplying power with the 5-V voltage source supplying 17.5 W.

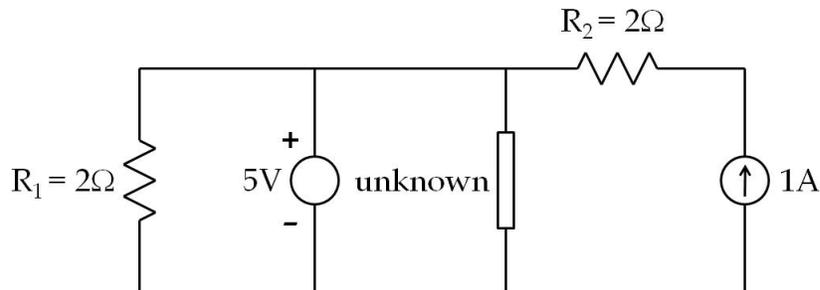


Figure 3. Determining the unknown device

- Calculate the power being absorbed by R_1 and R_2 .
- Calculate the power being supplied by the 1-A current source.
- Is the unknown device absorbing or supplying power?

- d. Identify two possible circuit elements for the unknown device.
3. Using nodal analysis, determine the power generated/absorbed by each of the sources in the circuit illustrated in Fig 4.

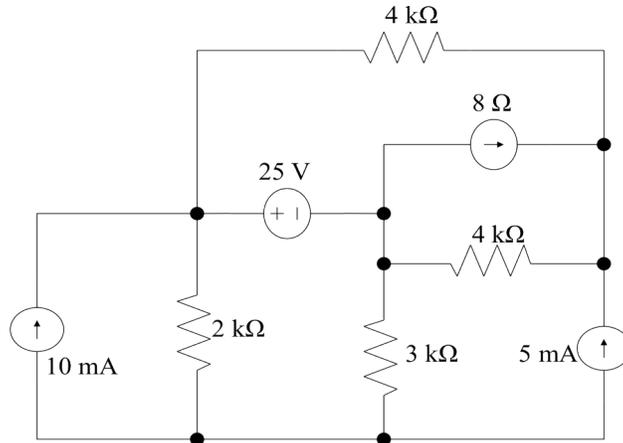


Figure 4. Using nodal analysis to determine the power generated

4. Express V_A and V_B as a function of your input V_{in} .

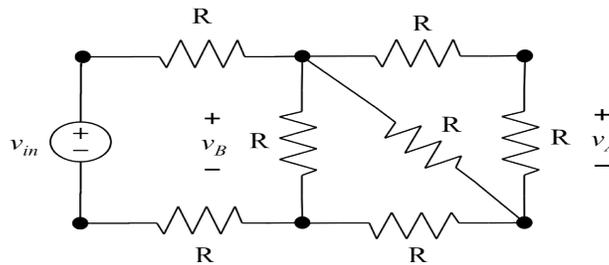


Figure 5. Expressing output functions

5. Determine the power generated by the 10V source.

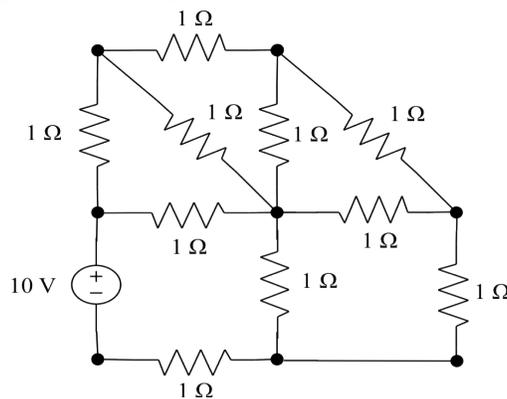


Figure 6. Computing power

6. Use the mesh-current method to find the total power being supplied in the circuit in Fig. 8.

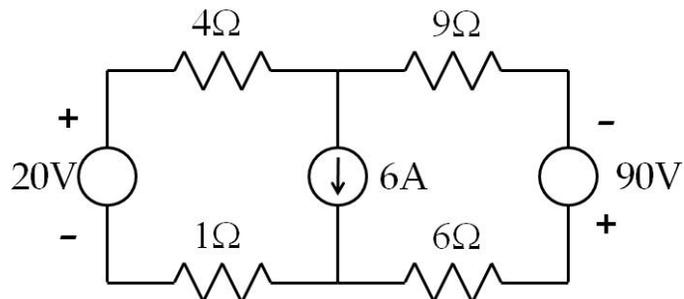


Figure 7. Using mesh-current method to find unknown power

7. (a) Use the mesh-current method to find v_0 in the circuit in Fig. 9.
 (b) Calculate the power being delivered by the dependent source.

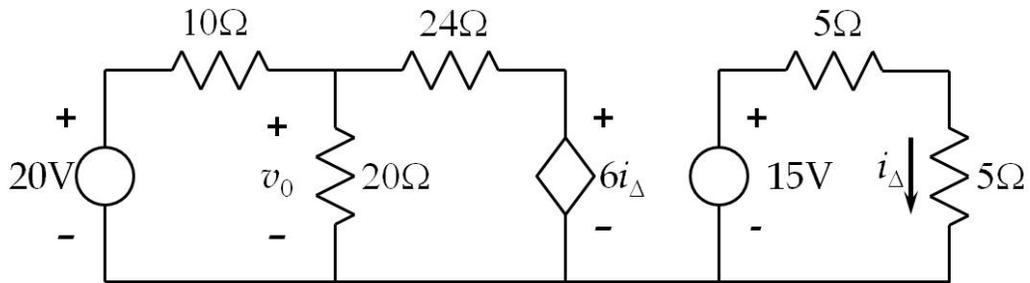


Figure 8. Using mesh-current method to find v_0

8. Using nodal analysis, find V_0 and I_0 in this circuit.

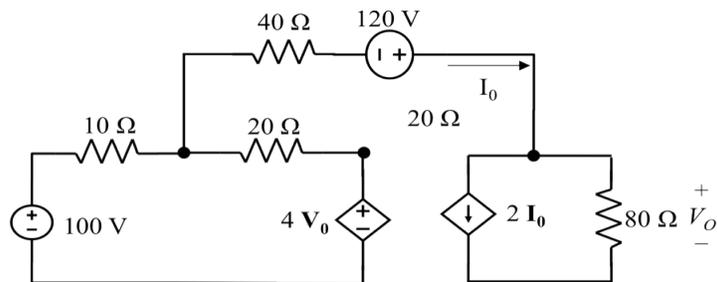


Figure 9. Using nodal analysis to find the unknown parameters