

EEE 31 Problem Set 1

Problem 1

Given the circuit in Figure 1.

- Find the equivalent resistance, R_{eq} , seen terminals A and B.
- If a 5V supply is connected at terminals A and B ($V_{AB} = 5V$), find V_{CD} and V_{EF} .

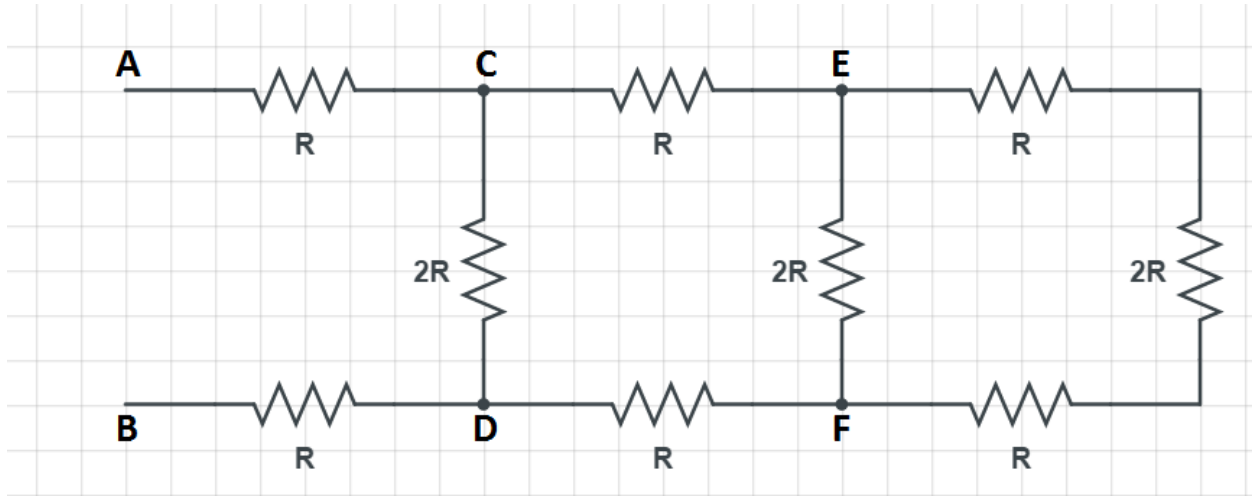


Fig.1

Problem 2

Given the circuit in Figure 2.

- Express V_4 in terms of V_s and the resistors.
- If $i_2 = 1A$, and $R_1 = R_2 = R_3 = R_4 = R_5 = 10 \Omega$, find the value of V_4 and V_s .

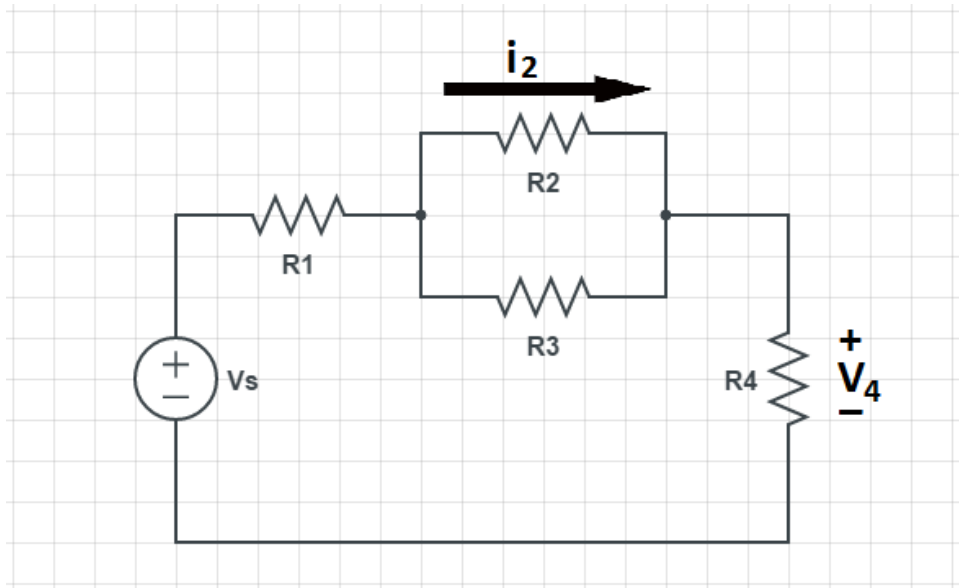


Fig. 2

Problem 3

A certain device has a V-I characteristics (Y-axis: Voltage, X-axis: Current) shown in Figure 3a. If a voltage shown in Figure 3b is applied to the device,

- Plot the current vs time of the device for $0 \leq t \leq 5$ s
- Calculate the total energy absorbed by the device from 0 to 5s.

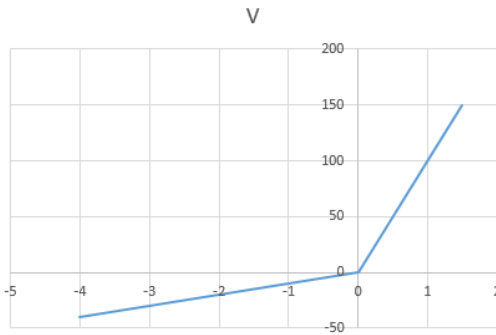


Fig. 3a

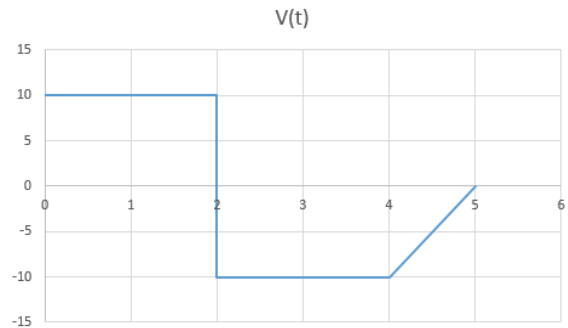


Fig. 3b

Problem 4

Given the circuit in Figure 4

- Find all the mesh currents i_A , i_B , and i_C
- Compute the power absorbed by all resistors.

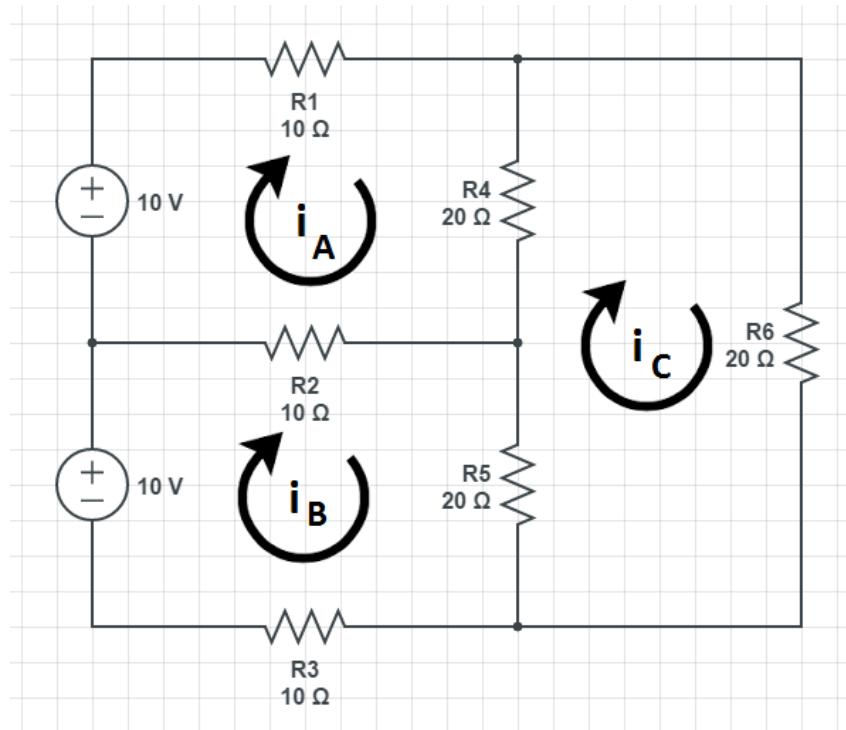


Fig. 4

Problem 5

Given the circuit in Figure 5, use node voltage analysis to get the voltages across all resistors.

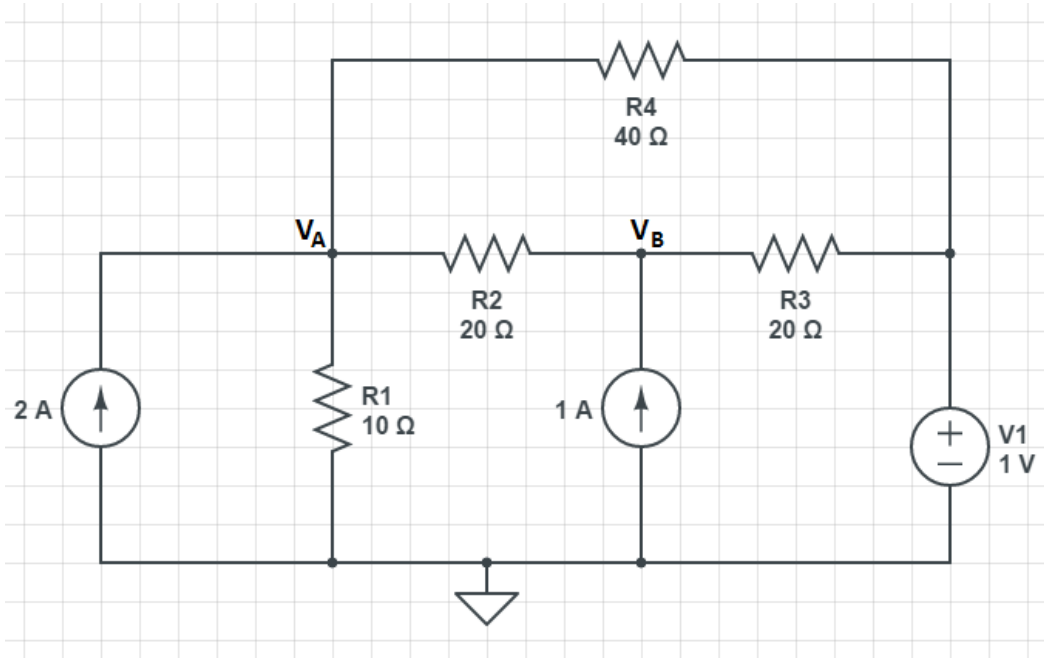


Fig. 5

Problem 6

Given the resistance network in Figure 6

- Find the equivalent resistance across A and B in terms of R.
- What value of R will result with an equivalent resistance of 10kΩ

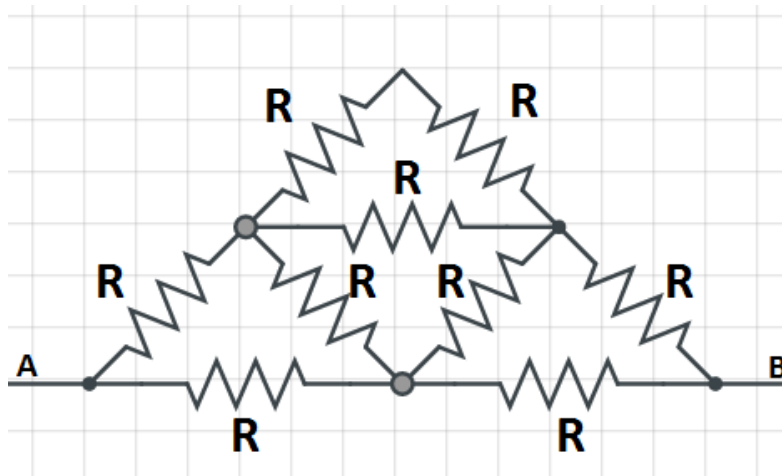


Fig. 6

Problem 7

Figure 7 shows a cube resistor. Assume that all resistors have a resistance of R .

- If a voltage V_s is applied across A and G ($V_s = V_{AG}$), what is the voltage V_B , V_C , V_D , V_E and V_F ? Use G as the reference node ($V_G = 0$). Express your answers in terms of R and V_s . (Hint: Use the cube's symmetry.)
- Find the value of R such that the equivalent resistance is $10\text{k}\Omega$.

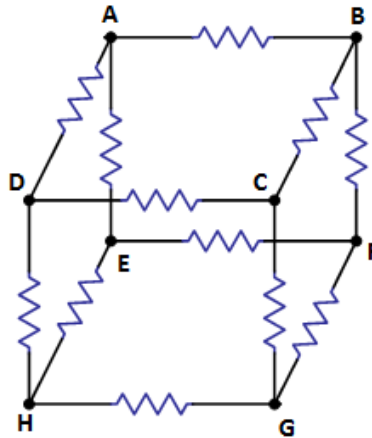


Fig. 7

Problem 8

Use mesh analysis to solve the circuit in Figure 8.

- Write down the mesh current equations for loops 3 and 4.
- Express i_1 in terms of i_2 .
- Find the value of all mesh currents.
- Find the value of V_x .

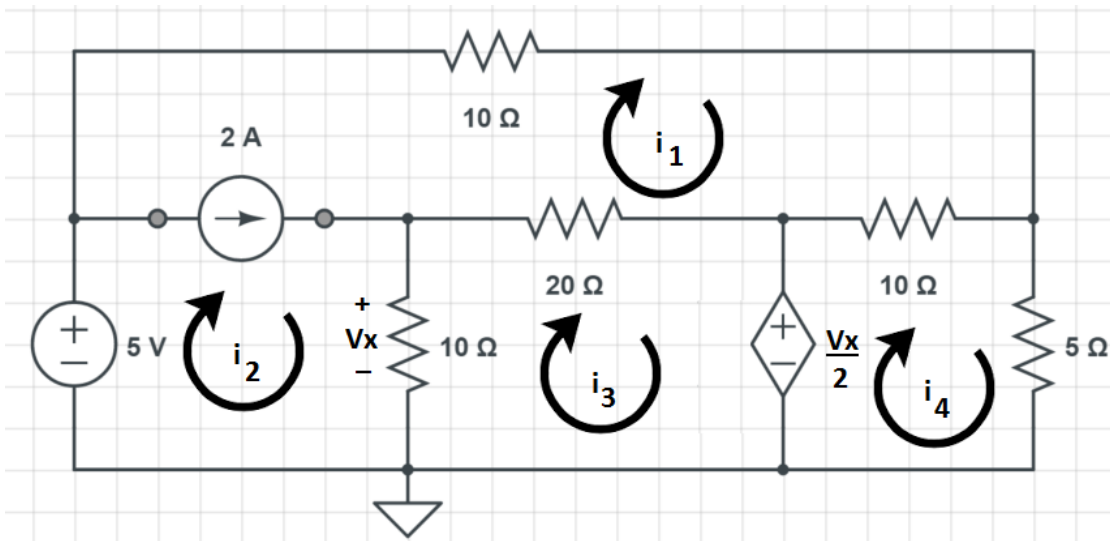


Fig. 8