

$$\begin{aligned}
 \textcircled{1} \text{ a. } R_{eq} &= 2R + 2R \parallel [2R + (2R \parallel 4R)] \\
 &= 2R + 2R \parallel [2R + \frac{4}{3}R] \\
 &= 2R + 2R \parallel [\frac{10}{3}R] \\
 &= 2R + \frac{5}{4}R
 \end{aligned}$$

$$\boxed{R_{eq} = \frac{13}{4}R = 3.25R}$$

$$\text{b. } V_{CD} = 5V \left( \frac{\frac{5}{4}R}{\frac{13}{4}R} \right)$$

$$\boxed{V_{CD} = \frac{25}{13}V = 1.923V}$$


$$\begin{aligned}
 V_{EF} &= V_{CD} \left( \frac{\frac{4}{3}R}{\frac{10}{3}R} \right) \\
 &= \frac{2}{5}V_{CD}
 \end{aligned}$$

$$\boxed{V_{EF} = \frac{10}{13}V = 0.769V}$$

$$\textcircled{2} \quad V_4 = V_{supply}$$

$$\text{a. } V_4 = V_s \left( \frac{R_4}{R_1 + R_2 \parallel R_3 + R_4} \right)$$
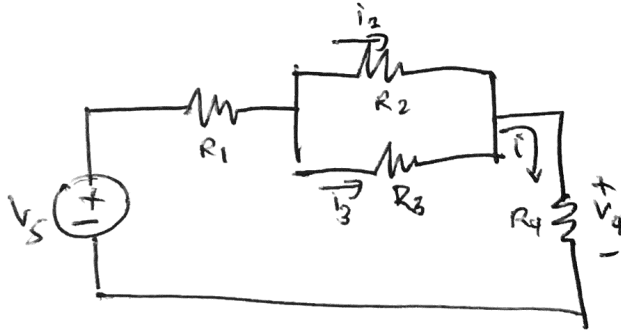
$$\boxed{V_4 = V_s \left( \frac{R_4}{R_1 + \frac{R_2 R_3}{R_2 + R_3} + R_4} \right)}$$



$$\text{b. } i_2 = i_3 = 1A$$

$$i_2 = i_3 = 1A$$

$$i_0 = i_2 + i_3 = 2i_2$$

$$i = 2A$$

$$V_4 = i(R_4)$$

$$= 2A(10)$$


$$\boxed{V_4 = 20V}$$

$$V_s = 2A(R_{eq})$$


$$= 2A(10\Omega + 5\Omega + 10\Omega)$$

$$\boxed{V_s = 50V}$$

③

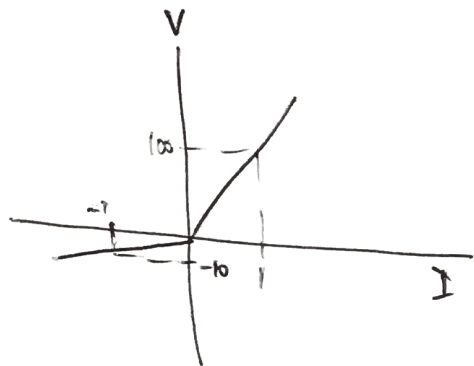
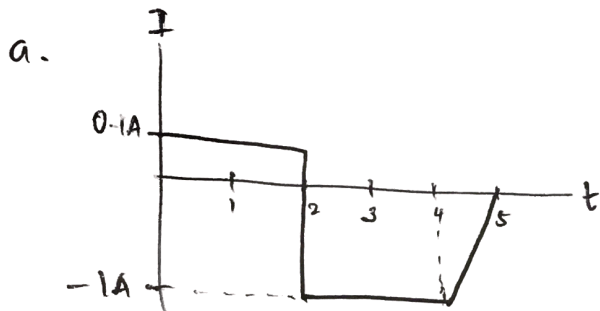
$$V = \begin{cases} 10I & \text{for } I \geq 0 \\ 10I & \text{for } I < 0 \end{cases}$$



b.  $P = VI$

$E = \int P dt \rightarrow$  area under the curve

$\approx P \Delta t$

$0 \leq t < 2s$

$I = 0.1A$

$V = 10V$

$P = 1W$

$E = 2J$

$2s \leq t < 4$

$I = -1A$

$V = -10V$

$P = 10W$

$E = 20J$

$4 \leq t \leq 5$ ; let  $t_0 = t - 4$

$V = -10 + 10t_0$

$I = -1 + t_0$

$E = \int_0^1 (-10 + 10t_0)(-1 + t_0) dt_0$

$= 10 \int_0^1 (-1 + t_0)^2 dt_0$

$= 10 \int_0^1 (1 - 2t_0 + t_0^2) dt_0$

$= 10 \left( t_0 - t_0^2 + \frac{t_0^3}{3} \right) \Big|_{t_0=0}^{t_0=1}$

$= 10 \left( 1 - 1 + \frac{1}{3} \right)$

$= \frac{10}{3} J$

$E = 2J + 20J + \frac{10}{3} J$

$E = 25\frac{1}{3} J$

(4)

a.

$$-10 + 10 i_A + 20(i_A - i_C) + 10(i_A - i_B) = 0$$

$$-10 + 10(i_B - i_A) + 20(i_B - i_C) + 10i_B = 0$$

$$20i_C + 20(i_C - i_B) + 20(i_C - i_A) = 0$$

simplifying:

$$4i_A - i_B - 2i_C = 1$$

$$-i_A + 4i_B - 2i_C = 1$$

$$-i_A - i_B + 3i_C = 0$$

$$\begin{aligned} i_A &= \frac{3}{5} \text{ A} = 0.6 \text{ A} \\ i_B &= \frac{3}{5} \text{ A} = 0.6 \text{ A} \\ i_C &= \frac{2}{5} \text{ A} = 0.4 \text{ A} \end{aligned}$$

b.  $P_{R1} = i_A^2 R_1$   
 $= (0.6)^2 (10)$

$$P_{R1} = 3.6 \text{ W}$$

$$P_{R2} = (i_A - i_B)^2 R_2$$

~~$$P_{R2} = 0$$~~

$$P_{R2} = 0$$

$$P_{R3} = i_B^2 R_3$$

$$P_{R3} = 3.6 \text{ W}$$

$$P_{R4} = (i_A - i_C)^2 R_4$$

$$= (0.2)^2 (20)$$

$$P_{R4} = 0.8 \text{ W}$$


$$P_{R5} = (i_B - i_C)^2 R_5$$

$$P_{R5} = 0.8 \text{ W}$$

$$P_{R6} = i_C^2 R_6$$

$$P_{R6} = 3.2 \text{ W}$$

(5)

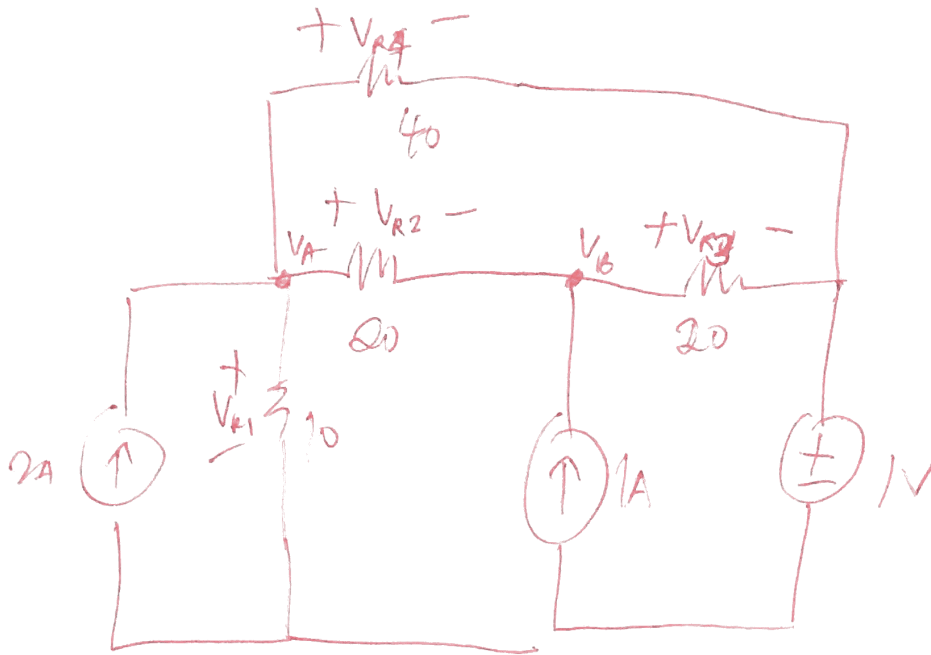

node A

$$-2 + \frac{V_A}{10} + \frac{V_A - V_B}{20} + \frac{V_A - 1}{40} = 0 \Rightarrow -80 + 4V_A + 2V_A - 2V_B + V_A - 1 = 0$$

$$7V_A - 2V_B = 81$$

node B

$$\frac{V_B - V_A}{20} - 1 + \frac{V_B - 1}{20} = 0 \Rightarrow 2V_B - V_A = 21$$

$$7V_A - 2V_B = 81$$

$$-V_A + 2V_B = 21$$

$$6V_A = 102$$

$$V_A = 17V$$

$$V_B = 19V$$



$$V_{R1} = 17V$$

$$V_{R2} = -2V \quad \text{or } 2V$$


$$V_{R3} = 18V$$

$$V_{R4} = 10V$$

6

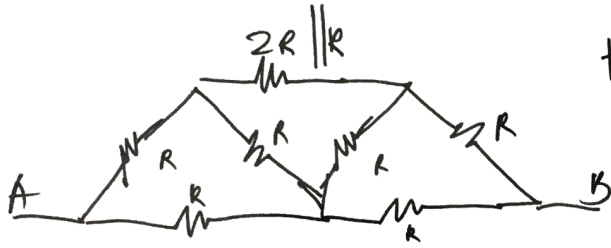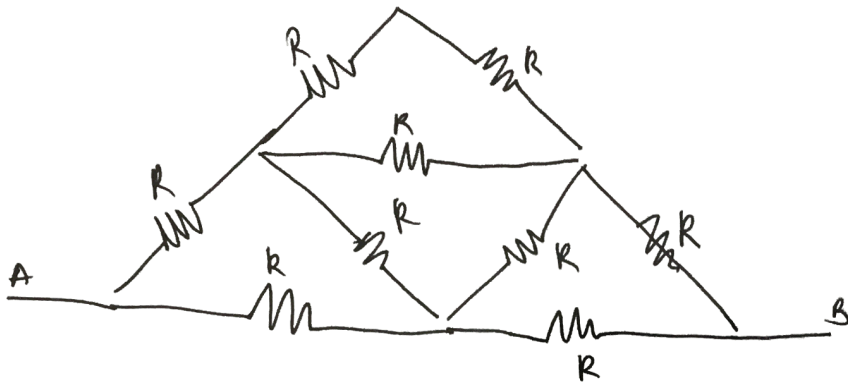

top part is simplified

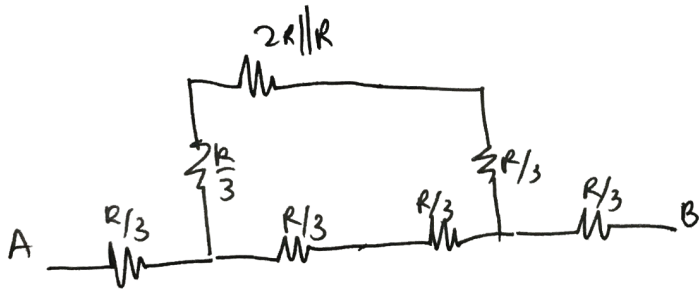

both deltas at the bottom are transformed to Y

a.)

$$R_{eq} = \frac{R}{3} + \left( \frac{R}{3} + 2R \parallel R + \frac{R}{3} \right) \parallel \left( \frac{R}{3} + \frac{R}{3} \right) + \frac{R}{3}$$

$$= \frac{2R}{3} + \frac{4R}{3} \parallel \frac{2R}{3}$$

$$= \frac{2R}{3} + \frac{4R}{9}$$


$$R_{eq} = \frac{10R}{9}$$

b.)  $R_{req} = R = \frac{9}{10} R_{eq}$

if  $R_{eq} = 10k\Omega$

$$R = 9k\Omega$$

7

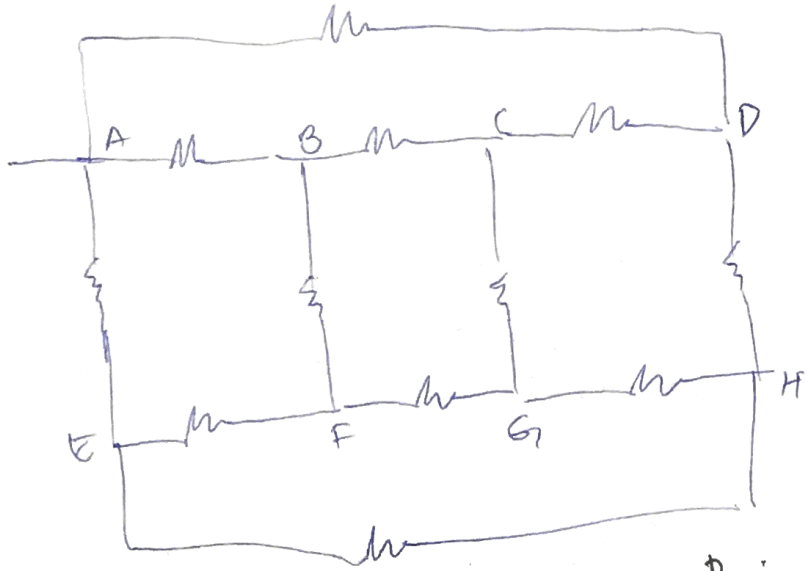

$V_A = V_S$   
 $V_G = 0$

Using symmetry of cube:

$V_B = V_D = V_E$

$V_C = V_F = V_H$

node voltage @ B

$$\frac{V_B - V_A}{R} + \frac{V_B - V_C}{R} + \frac{V_B - V_F}{R} = 0$$

$3V_B - V_C - V_F = V_A = V_S$   
 $3V_B - 2V_C = V_S$

node voltage @ C

$$\frac{V_C - V_B}{R} + \frac{V_C - V_D}{R} + \frac{V_C - V_G}{R} = 0$$

$3V_C = V_B + V_D$   
 $3V_C = 2V_B$   
 $V_C = \frac{2}{3}V_B$


$3V_B - 2(\frac{2}{3}V_B) = V_S$

$\frac{5}{3}V_B = V_S$

$V_B = V_E = V_D = \frac{3}{5}V_S$

$V_C = V_F = V_H = \frac{2}{5}V_S$

Req:

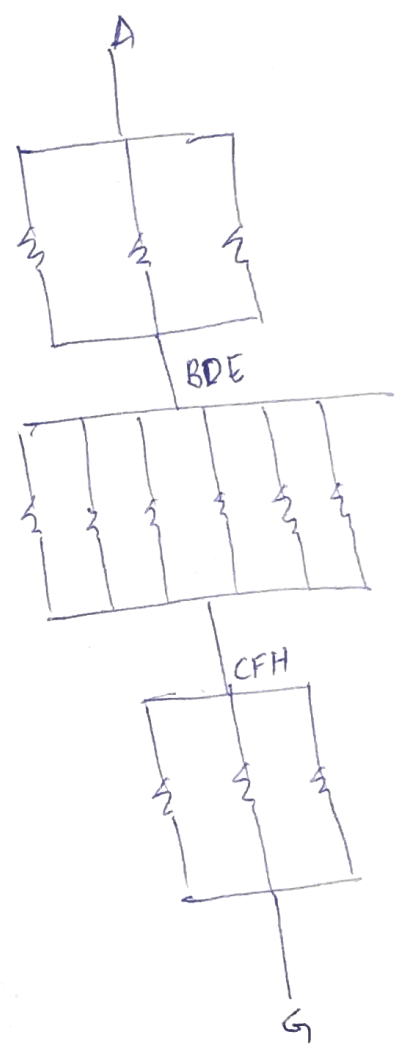

$Req = (R||R||R) + (R||R||R||R||R||R) + (R||R||R)$

$= \frac{R}{3} + \frac{R}{6} + \frac{R}{3}$

$= \frac{5}{6}R \rightarrow 10k = \frac{5}{6}R \quad R = 12k\Omega$

8

a. loop 3:

$$20(i_3 - i_1) + \underbrace{\frac{V_x}{2} - V_x}_{-V_x/2} = 0$$

$$\begin{aligned} -V_x &= 10(i_3 - i_2) \\ V_x &= 10(i_2 - i_3) \end{aligned}$$

$$20(i_3 - i_1) - \frac{10}{2}(i_2 - i_3) = 0$$

$$\text{Eq. 1: } -20i_1 - 5i_2 + 25i_3 = 0$$

loop 4:

$$-\frac{V_x}{2} + 10(i_4 - i_1) + 5i_4 = 0$$

$$-5(i_2 - i_3) + 10(i_4 - i_1) + 5i_4 = 0$$

$$\text{Eq. 2: } -10i_1 - 5i_2 + 5i_3 + 15i_4 = 0$$

b. ~~2A = 2A~~

$$\text{Eq. 3: } i_2 - i_1 = 2A$$

$$\boxed{i_1 = i_2 - 2}$$

c. Eq. 4: outer most loop

~~$$-5 + 10i_1 + 5i_4 = 0$$~~

$$\text{Eq. 4: } 2i_1 + i_4 = 1$$

$$\begin{aligned} i_1 &= \frac{7}{40} A = 0.175 A \\ i_2 &= \frac{87}{40} A = 2.175 A \\ i_3 &= \frac{23}{40} A = 0.575 A \\ i_4 &= \frac{13}{20} A = 0.65 A \end{aligned}$$

$$\begin{aligned} V_x &= 10(i_2 - i_3) \\ &= 10(2.175 A - 0.575 A) \end{aligned}$$

$$\boxed{V_x = 16V}$$