

EEE 31 Problem Set 1

Due:

1. Calculate the equivalent resistance R_{eq} of the network shown in Figure 1 below if $R_1 = 2R_2 = 3R_3 = 4R_4$, etc and $R_{11} = 3 \Omega$.

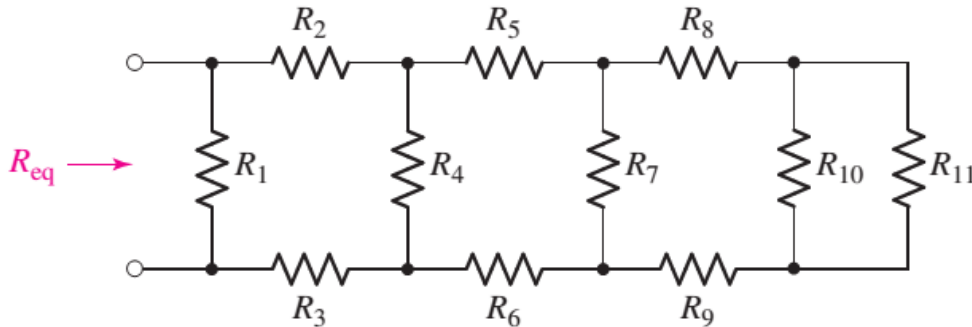


Figure 1

2. In the Figure 2 below, only the voltage v_x is of interest. Simplify the circuit using the appropriate resistor combinations and iteratively employ voltage division to determine v_x .

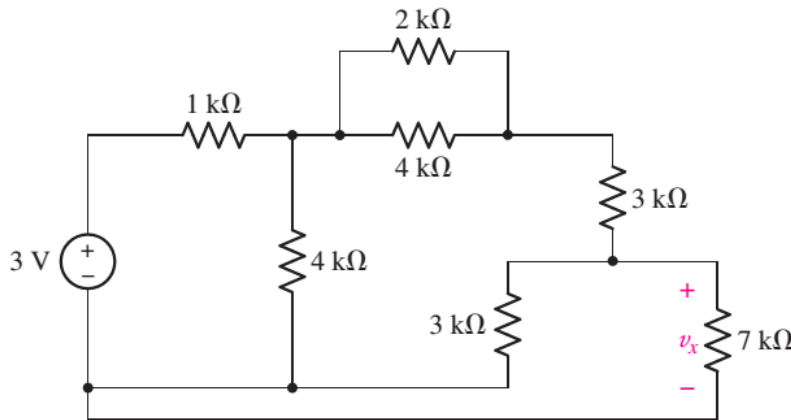


Figure 2

3. The $600 \text{ k}\Omega$ resistor is connected from the 200 V terminal to the common terminal of a dual-scale voltmeter, as shown in Figure 3.(a) below. This modified voltmeter is then used to measure the voltage across the $360 \text{ k}\Omega$ resistor in the circuit in Figure 3.(b).

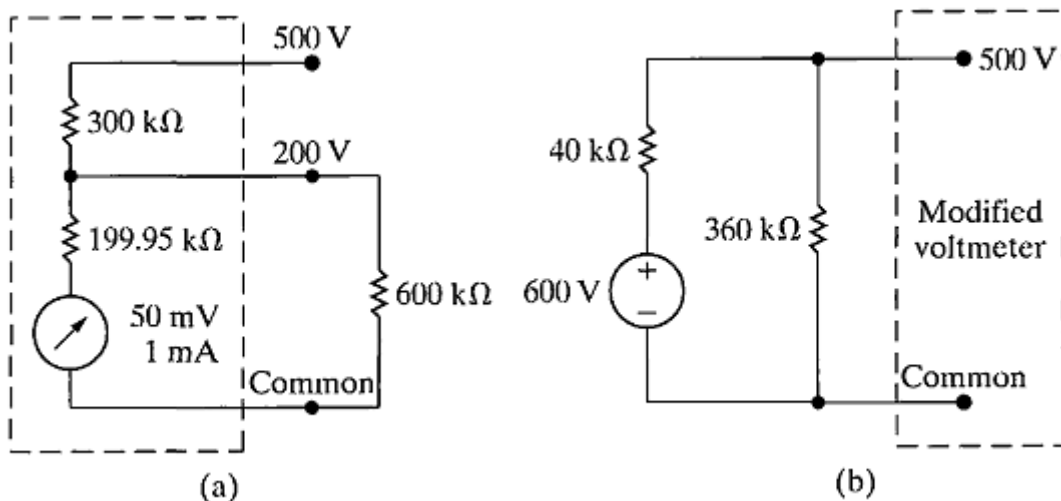


Figure 3

EEE 31 Problem Set 1

Due:

- a. What is the reading on the 500 V scale of the voltmeter?
 - b. What is the percentage error in the measured voltage?
4. Use Y-to- Δ transformation to find i_1 , i_2 and i_o and the power delivered by the ideal current source in the Figure 4 below.

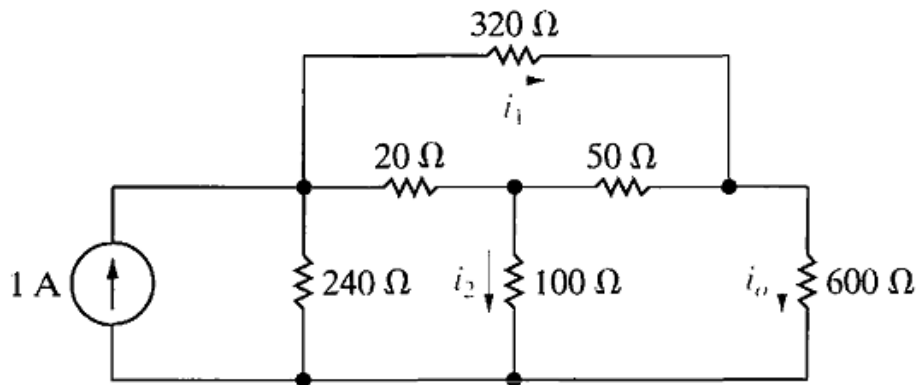


Figure 4.

5. Using the bottom node as reference, determine the voltage across the 5 Ω resistor in the Figure 5 below, and calculate the power dissipated by the 7 Ω resistor.

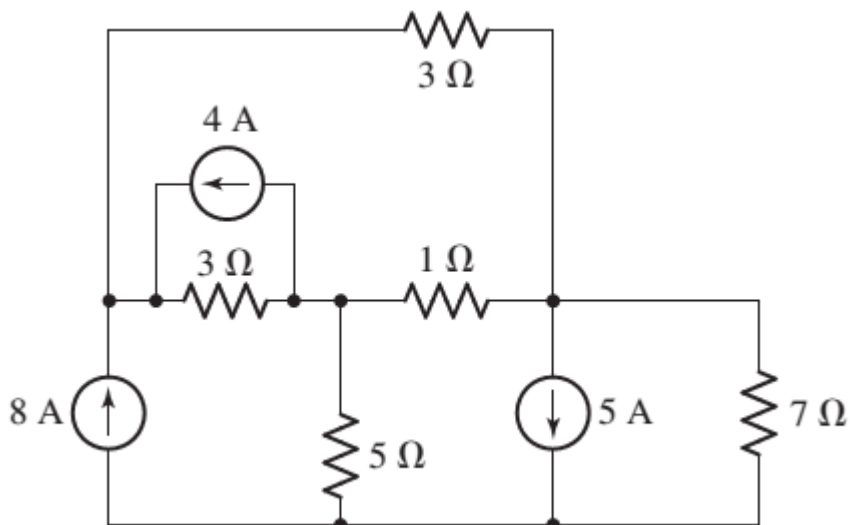


Figure 5

6 Problem 6

In circuit experiments, it is helpful to have a visual indication of circuit activity. A light emitting diodes (LED) is a circuit element that emits light when current passes through it. An LED is often used in a circuit to give that visual indication. The circuit symbol for an LED is shown below. When current passes through the LED, we can approximate the LED as a 1 V source in series with a $10\ \Omega$ resistance as shown in the LED model below. A commonly used LED has a maximum current rating of 30 mA.

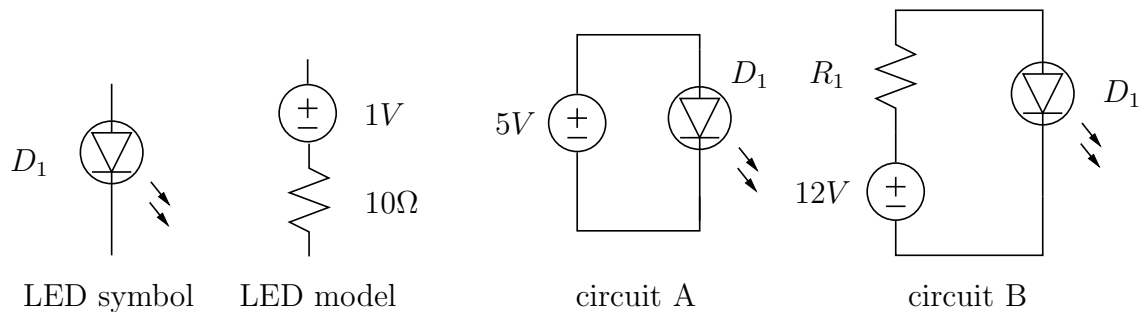


Figure 1:

- To test LEDs, students often haphazardly connect the LED as shown in circuit A. Is this a good idea? Why or why not?
- In circuit B, what is the range of values for R_1 that would avoid the failure of the LED.
- If the single LED in circuit B is replaced by two LEDs (pointing in the same direction) in series, what is the range of values of R_1 that would avoid LED failure.

7 Problem 7

A gasoline powered vehicle traveling at a constant speed of 100 km/hr can go 15 km for every liter of gasoline. Gasoline has an energy density of 32.4 MJ/liter. A gasoline powered vehicle has an overall "tank-to-wheel" efficiency of about 25%, i.e., only 25% of the energy content of the gasoline is converted into usable power to move the vehicle; the rest is lost to heat.

An electric powered vehicle uses energy stored in batteries to power an electric motor that eventually drives the vehicle. An electric vehicle has a "battery-to-wheel" efficiency of about 85%. However, before an electric vehicle can be used, the batteries must first be charged from a power outlet. The charging operation is around 80% efficient.

- If electricity cost P10 per kW-hr, how much does a liter of fuel need to cost in order for the fuel cost of running the gasoline vehicle to be the same as the electricity cost of running the electric vehicle.
- How much power does the electric motor deliver when the vehicle is running at 100 km/hr? How much power is being drawn from the batteries at this speed?
- If the battery voltage is 300 V, how much current is drawn from the batteries at 100 km/hr? If the electric vehicle has a 40 ampere-hour battery, what distance can it travel on a full charge?

8 Problem 8

Shown in Figure 2 are the plots for voltage and current for device B. Plot the power absorbed by device B vs. time, the energy absorbed vs. time. What is the total energy absorbed by device B after 3 hours?

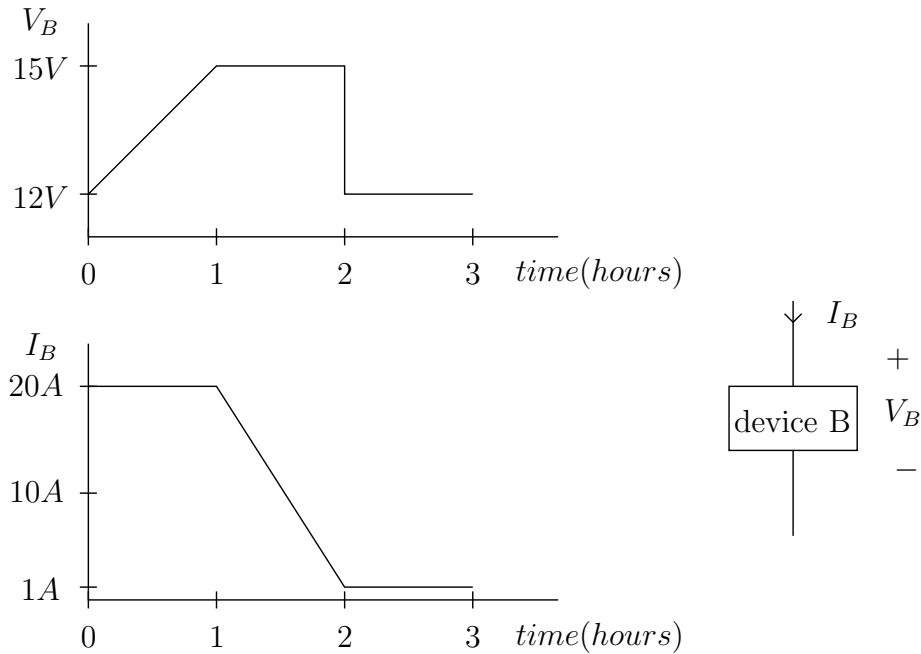


Figure 2:

9 Problem 9

Given the circuit in Figure 3.

- Solve for the value of load voltage V_L that will give maximum power to the load in terms of R_1 and R_2 .
- If $R_1 = 2\Omega$ and $R_2 = 1\Omega$, what is V_L for maximum power?

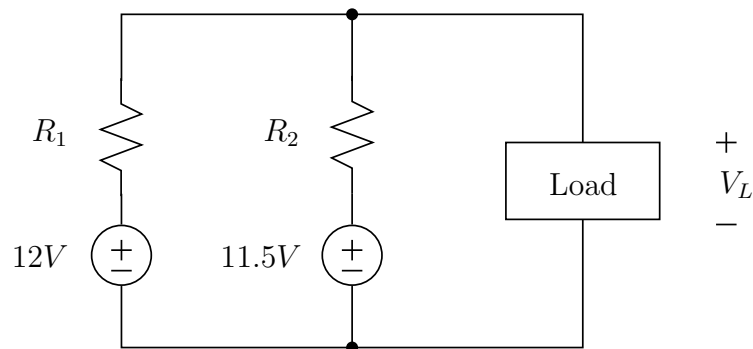


Figure 3:

10 Problem 10

Refer to the circuit in Figure 4. Solve for V_R using only KCL, KVL and Ohm's law. Clearly write down your solution.

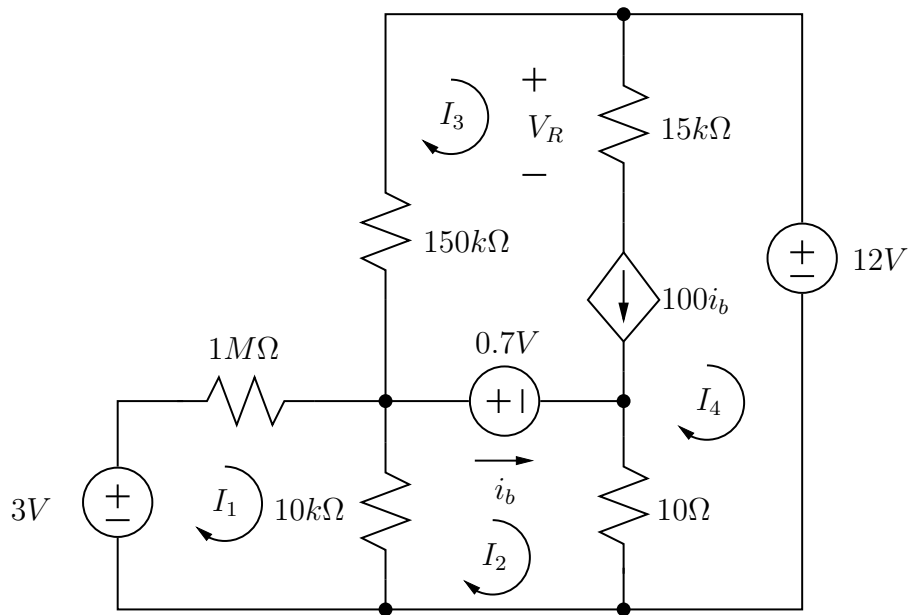


Figure 4:

11 Problem 11

Refer to the circuit in Figure 4.

- Solve for V_R using the node voltage method. Setup your equations clearly.
- Solve for V_R using the mesh analysis method. Setup your equations clearly.