

EEE 31 Problem Set 2
 Due: Jan 31, 2012 (5pm)

1. Use node-voltage method to calculate the power being dissipated by the 2- Ω resistor for the circuit in Fig. 1.

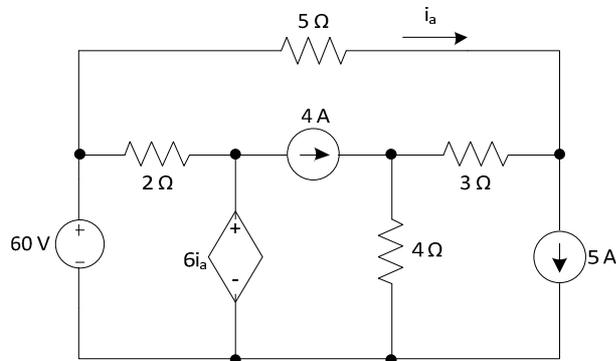


Fig. 1

2. Use mesh-current method to calculate the power being dissipated by the 2- Ω resistor for the circuit in Fig. 1.
3. Find the Thevenin and Norton equivalent with respect to the terminals a,b for the circuit shown in Fig. 2.

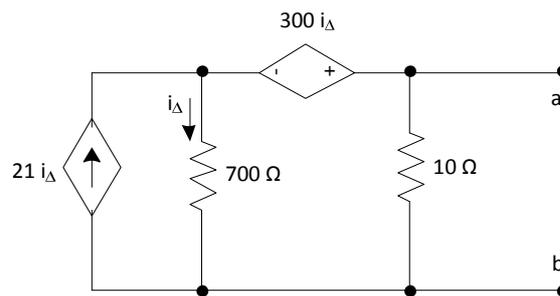


Fig. 2

4. For the given circuit in Fig. 3

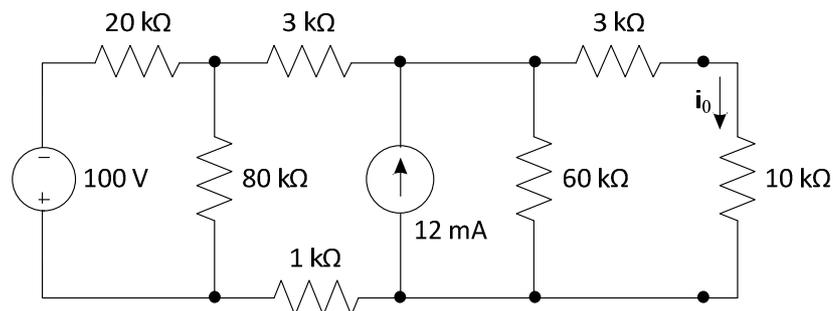


Fig. 3

- a. Find the current in the 10 k Ω resistor by using successive source transformations.
- b. Using the results in a), work back through the circuit to find the power developed in the 100 V source.