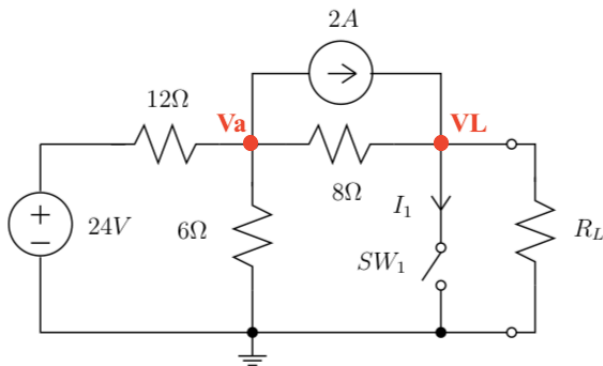


EEE 31 Problem Set 2 Answer Key

1. Consider node  $V_a$  and  $V_L$ ,



For maximum power transfer,  $R_L$  should be equal to  $R_{TH}$  seen by the load when the switch is open.

$$R_{TH} = 8 + 12 || 6 \Omega = 12 \Omega = R_L$$

The voltage across the load can be computed using (1) and (2):


$$\frac{V_a - 24}{12\Omega} + \frac{V_a}{6\Omega} + \frac{V_a - V_L}{8\Omega} + 2 = 0 \quad (1)$$

$$\frac{V_L - V_a}{8\Omega} + \frac{V_L}{R_L} = 2 \quad (2)$$

Two equations two unknowns,  $V_L = 12V$ .

$$P_L = \frac{V_L^2}{12} = 12W$$

2.

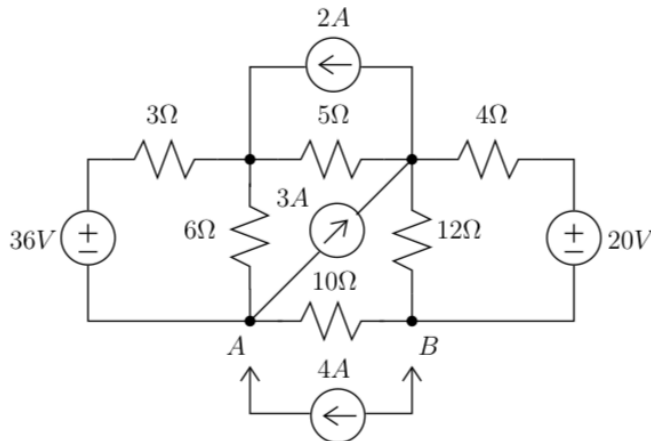

Without 4A connected:


$$V_{th,ab} = 10V$$

$$R_{th,ab} = (3 || 6 + 5 + 4 || 12) || 10 = 5\Omega$$

When 4A source is connected,

$$V_{ab} = (10 + 5 * 4)V = 30V$$

3.

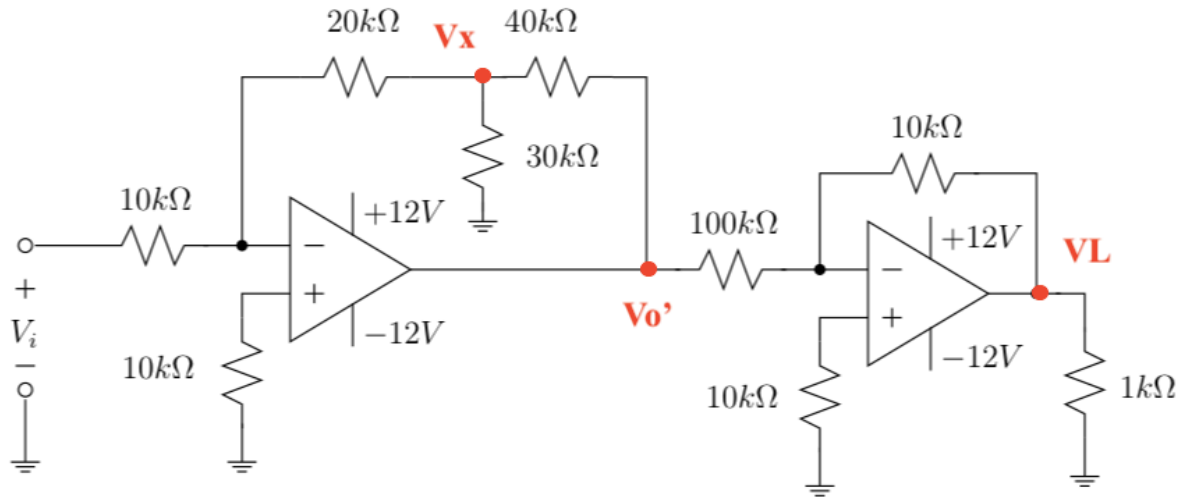

The first half of the circuit will give a gain of:

$$\frac{0 - V_i}{10k\Omega} + \frac{0 - V_x}{20k\Omega} = 0, \quad \frac{V_x - 0}{30k\Omega} + \frac{V_x - 0}{20k\Omega} + \frac{V_x - V_o'}{40k\Omega} = 0$$

$$V_o' = -\frac{26}{3}V_i = -13V$$

$$V_o' = -13V \rightarrow -12V$$


Combine with the gain of the second circuit:

$$\frac{0 - V_o'}{100k\Omega} + \frac{0 - V_L}{10k\Omega} = 0$$

$$V_L = -\frac{1}{10}V_o' \rightarrow V_L = -\frac{1}{10}(-12) = 1.2V$$

$$P_L = \frac{(1.2)^2}{1000\Omega} = 1.44mW$$

4.

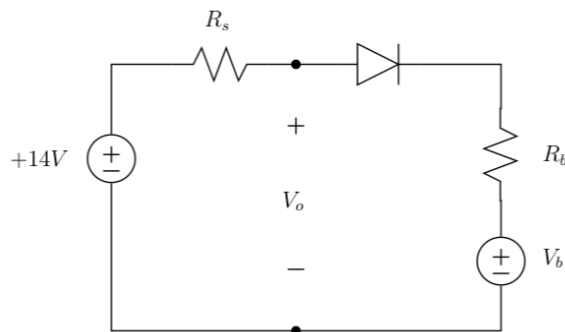

For an ideal diode, turn-on voltage is 0V. Let current  $I$  to be the current around the circuit.

Case 1:

Consider  $V_b > 14V$

$$V_{diode} = (14 - IR_s) - (V_b + IR_b)$$

For small  $R_s$  and  $R_b$ , we are sure that:

$$V_{diode} < 0V \therefore \text{Diode is open}$$

$$V_o = 14V - 0R_s = 14V$$

Case 2:

Consider  $V_b \leq 14V$

$$V_{diode} = (14 - IR_s) - (V_b + IR_b)$$

For small  $R_s$  and  $R_b$ , we are sure that:

$$V_{diode} \geq 0V \therefore \text{Diode is shorted}$$

$$V_o = 14V - IR_s = V_b + IR_b$$

Current  $I$  is always positive:

$$V_o \leq 14V$$