
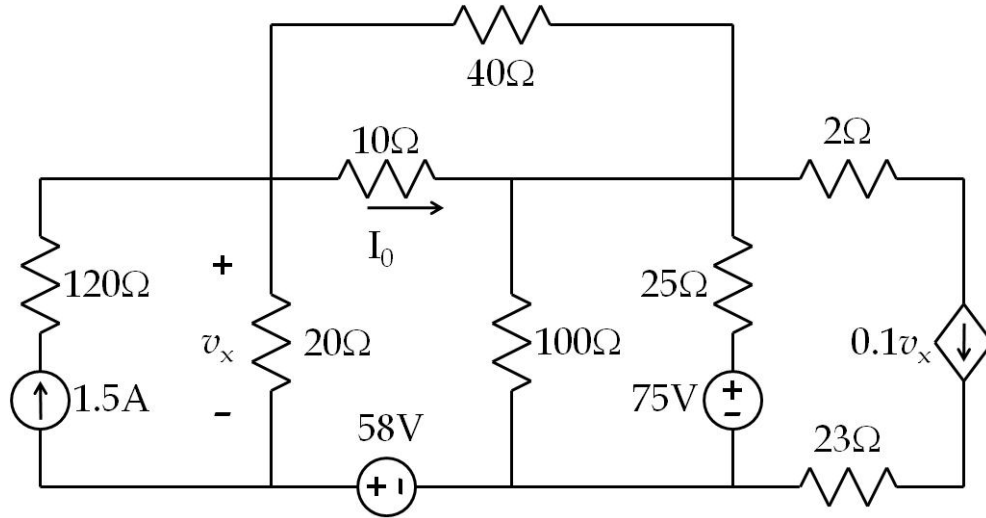


EEE 31  
 Problem Set 2 Part 1

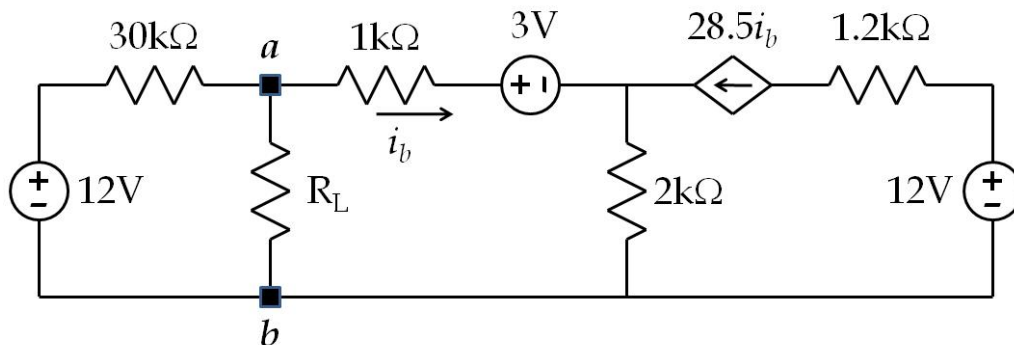
1. Using a series of source transformations, simplify the circuit to a single KVL or KCL problem and solve for  $v_x$  and  $I_0$ .



2. For the given circuit below, find the following:  
 a. the Thevenin equivalent as seen by the load  $R_L$   
 b. the maximum power that can be delivered to the load  
 c. the value of  $R_L$  if  $R_L$  absorbs half of the maximum power (*your answer in b*)



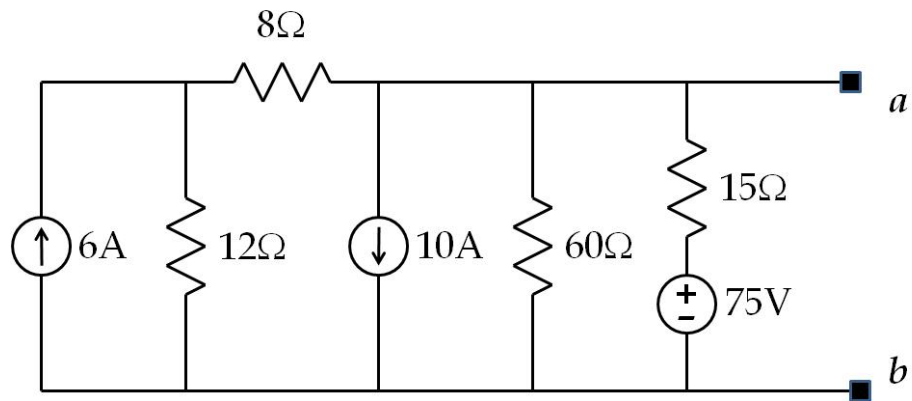3. Determine the Norton equivalent across terminals *a* and *b*. Note that for this problem, you are allowed to use source transformation just once on any part of the circuit.



4. Use the principle of superposition to solve for  $V_0$ .

