

# EEE 31 Problem Set 2 Part I

## 1 Part 1 Prob 1

### 1.1 Using source transformations

Left-side of variable Resistance (R)

$$\begin{aligned}
 I_{s, \text{left}} &= \frac{15}{300} \\
 R_{s, \text{left}} &= 300 \parallel 150 \\
 &= \frac{(300)(150)}{300 + 150} \\
 &= 100\Omega \\
 V_{s, \text{left}} &= \frac{(15)(100)}{300} \\
 &= 5V
 \end{aligned}$$

Right-side of variable Resistance (R)

$$\begin{aligned}
 I_{s, \text{right}} &= \frac{40}{120} \\
 R_{s, \text{right}} &= 120 \parallel 480 \\
 &= \frac{(120)(480)}{120 + 480} \\
 &= 96\Omega \\
 V_{s, \text{right}} &= \frac{(40)(96)}{120} \\
 &= 32V
 \end{aligned}$$

$$\begin{aligned}
 V_{Th} &= 32 - 5 \\
 &= 27V \\
 R_{Th} &= 100 + 96 \\
 &= 196\Omega \\
 P_{max} &= \frac{\left(\frac{27}{2}\right)^2}{196}
 \end{aligned}$$

### 1.2 Using Mesh Current Method

Thevenin Voltage (higher potential at the right terminal)

$$\begin{aligned}
 V_{Th} &= 40 \frac{480}{480 + 120} - 15 \frac{150}{150 + 300} \\
 &= 32 - 5 \\
 &= 27V
 \end{aligned}$$

Thevenin Resistance

$$\begin{aligned}
 R_{Th} &= (300 \parallel 150) + (480 \parallel 120) \\
 &= 196\Omega
 \end{aligned}$$

## 2 Part 1 Prob 2

To get the Thevenin equivalent, remove  $R_L$ , then analyze across that terminal-pair

### 2.1 Using Superposition

With voltage source acting alone

$$\begin{aligned} i_x &= 10i_x \\ i_x &= 0 \\ V'_{OC} &= 3(10i_x) \\ V'_{OC} &= 0 \\ I'_{SC} &= 10i_x \\ &= 0A \end{aligned}$$

With current source acting alone

$$\begin{aligned} i_x + 0.9 &= 10i_x \\ i_x &= 0.1A \\ V''_{OC} &= 3(10i_x) \\ V''_{OC} &= 3V \\ I''_{SC} &= 10i_x \\ &= 1A \end{aligned}$$

$$\begin{aligned} V_{OC} &= 0 + 3 \\ &= 3V \\ I_{SC} &= 0 + 1 \\ &= 1A \\ R_{Th} &= 3\Omega \end{aligned}$$

### 2.2 Using KCL

$$\begin{aligned} i_x + 0.9 &= 10i_x \\ i_x &= 0.1A \\ V_{OC} &= 3(10i_x) \\ &= 3V \\ I_{SC} &= 10i_x \\ &= 1A \\ R_{Th} &= 3\Omega \end{aligned}$$

For maximum power transfer:

$$\begin{aligned} R_L &= R_{Th} \\ &= 3\Omega \\ P_{max} &= \frac{\left(\frac{3}{2}\right)^2}{3} \\ &= 0.75W \end{aligned}$$

## 3 Part 1 Prob 3

### 3.1 Calculating $I_0$

Remove center  $1k\Omega$  resistor, then get the open circuit voltage ( $V_{OC}$ ), higher potential at the left terminal. Using Node Voltage Method with bottom node as reference, top node as  $V_1$ , center left node as  $V_2$  and center right node as  $V_3$ .

$$\begin{aligned}
\frac{V_1 - 12}{2k} + \frac{V_1 - V_2}{1k} + \frac{V_1 - 4}{2k} &= 2m \\
\frac{V_2 - V_1}{1k} &= 2I_x \\
I_x &= \frac{V_3}{1k} \\
2m + \frac{V_3}{1k} &= 0 \\
V_3 &= -2V \\
V_2 &= 2V \\
V_{OC} &= V_2 - V_3 \\
V_{OC} &= 4V
\end{aligned}$$

Replace center  $1k\Omega$  resistor with short circuit, then get the Norton current by calculating the short circuit current ( $I_{SC}$ ) to the right. Using Node Voltage Method with bottom node as reference, top node as  $V_1$ , and center node as  $V_2$ .

$$\begin{aligned}
\frac{V_1 - 12}{2k} + \frac{V_1 - V_2}{1k} + \frac{V_1 - 4}{2k} &= 2m \\
\frac{V_2 - V_1}{1k} + \frac{V_2}{1k} + 2m &= 2I_x \\
I_x &= \frac{V_2}{1k} \\
V_1 &= 2V \\
V_2 &= -4V \\
I_{SC} &= 2m + \frac{V_2}{1k} \\
I_N &= -4mA
\end{aligned}$$

$$\begin{aligned}
R_N &= \frac{V_{OC}}{I_{SC}} \\
&= -1k\Omega
\end{aligned}$$

### 3.2 Calculating $V_0$

Remove right  $2k\Omega$  resistor, then get the Thevenin voltage as open circuit voltage ( $V_{OC}$ ), higher potential at top terminal. Using Node Voltage Method with bottom node as reference, top node as  $V_1$ , center left node as  $V_2$  and center right node as  $V_3$ .

$$\begin{aligned}
\frac{V_1 - 12}{2k} + \frac{V_1 - V_2}{1k} &= 2m \\
\frac{V_2 - V_1}{1k} + \frac{V_2 - V_3}{1k} &= 2I_x \\
I_x &= \frac{V_3}{1k} \\
\frac{V_3 - V_2}{1k} + \frac{V_3}{1k} &= -2m \\
V_1 &= -4V \\
V_{OC} &= V_1 - 4 \\
V_{Th} &= -8V
\end{aligned}$$

Replace right  $2k\Omega$  resistor with short circuit, then calculate the short circuit current downwards. Using Node Voltage Method with bottom node as reference, top node as  $V_1$ , center left node as  $V_2$  and center right node as  $V_3$ .

$$\begin{aligned}
 \frac{V_1 - 4}{1k} + \frac{V_2 - V_3}{1k} &= 2I_x \\
 I_x &= \frac{V_3}{1k} \\
 2m + \frac{V_3}{1k} + \frac{V_3 - V_2}{1k} &= 0 \\
 V_2 &= 2V \\
 V_3 &= 0V \\
 I_{SC} &= 2m + \frac{V_2 - V_1}{1k} + \frac{12 - V_1}{2k} \\
 I_N &= 4mA
 \end{aligned}$$

$$\begin{aligned}
 R_{Th} &= \frac{V_{OC}}{I_{SC}} \\
 &= -2k\Omega
 \end{aligned}$$

#### 4 Part 1 Prob 4

$$\begin{aligned}
 V_{out1} &= -V_1 \\
 V_{out2} &= \frac{V_2}{2} \\
 V_{out3} &= 2V_3 \\
 V_o &= \frac{-120k}{40k}V_{out1} + \frac{-120k}{120k}V_{out2} + \frac{-120k}{30k}V_{out3} \\
 V_o &= 3V_1 - 0.5V_2 - 8V_3
 \end{aligned}$$

#### 5 Part 1 Prob 5

$$\begin{aligned}
 V_a &= -12V \\
 V_b &= -12 \left( \frac{20k}{40k + 20k} \right) \\
 &= -4V \\
 V_c &= V_b \\
 &= -4V \\
 V_d &= V_c \\
 V_d &= -4V \\
 \frac{V_d - V_e}{20k} + \frac{V_d - V_f}{20k} &= 0 \\
 \frac{V_g - V_f}{20k} + \frac{V_g}{40k} &= 0 \\
 V_g &= V_e \\
 V_e &= -\frac{16}{5}V \\
 V_f &= -\frac{24}{5}V
 \end{aligned}$$