

**Deadline: March 24, 2014 12NN**

Answer the following questions in a separate sheet. Provide your solution to each problem completely. State all your assumptions.

1. The circuit shown in Fig. 1 has an input current source  $i_s$ . Show that the output is proportional to this input.

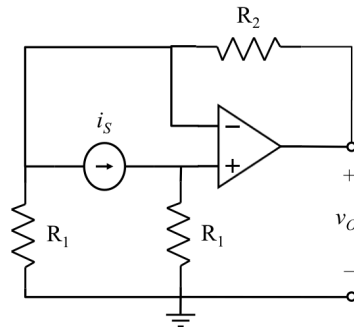


Figure 1

2. Find  $v_o$  and  $i_o$  for the circuit shown in Fig. 2.

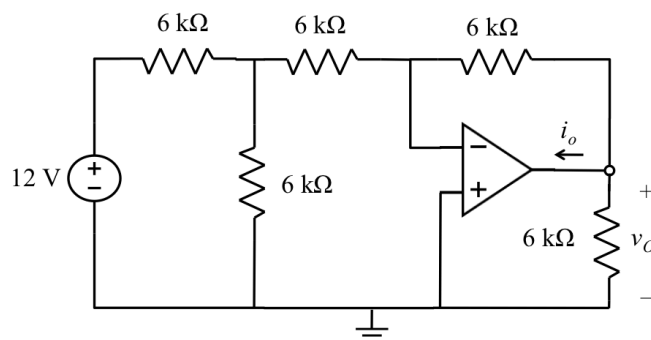


Figure 2

3. Design the circuit in Fig. 3 so that  $v_o = 20v_s$ .

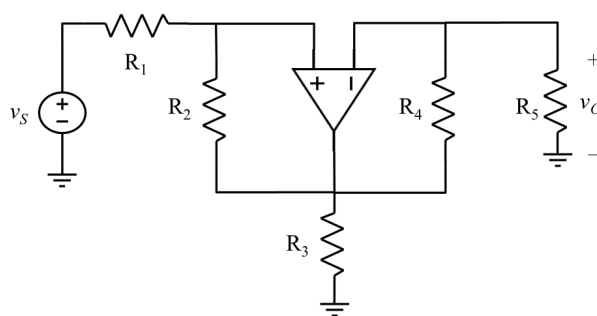


Figure 3

4. Find  $v_o/v_s$  in Fig. 4.

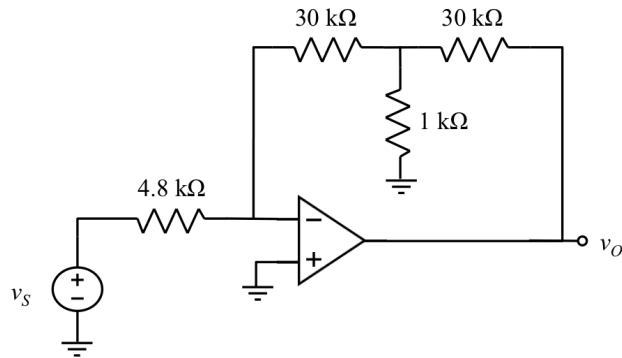


Figure 4

5. The capacitor voltage in the circuit shown below is:

$$v(t) = 2.4 + 5.6e^{-5t} \text{ V for } t \geq 0.$$

Determine the voltage  $i(t)$   $t > 0$ .

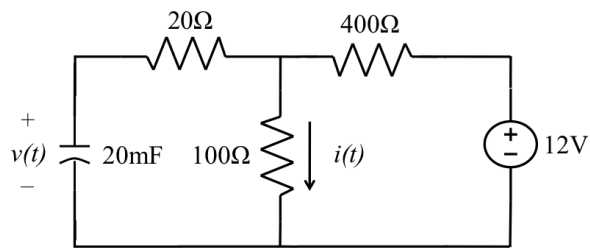


Figure 5

6. The inductor current in the circuit shown below is:

$$i(t) = 3 + 2e^{-3t} \text{ A for } t \geq 0.$$

Determine the voltage  $v(t)$   $t > 0$ .

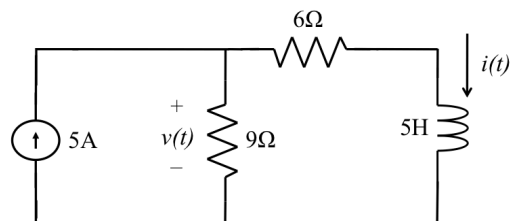


Figure 6