

Problem 1: Determine R_{AB} in the circuit in Fig. P2.46.

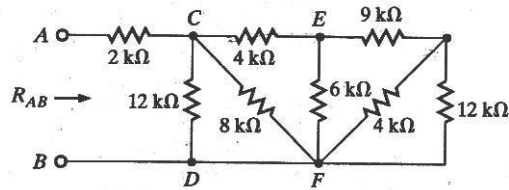


Figure P2.46

Problem 2: If $V_o = 2\text{ V}$ in the circuit in Fig. P2.57, find V_s .

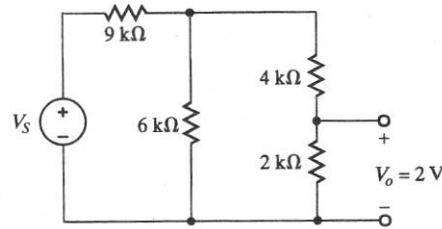


Figure P2.57

Problem 3: If the power absorbed by the 4-kΩ resistor in the circuit in Fig. P2.58 is 36 mW find I_o .

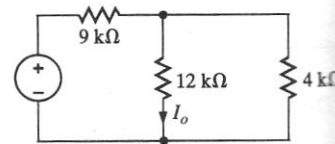


Figure P2.58

Problem 4: Find V_o in the network in Fig. P2.63.

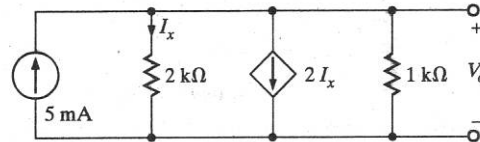


Figure P2.63

Problem 5: Find V_o in the network in Fig. P3.46 using both mesh and nodal analysis.

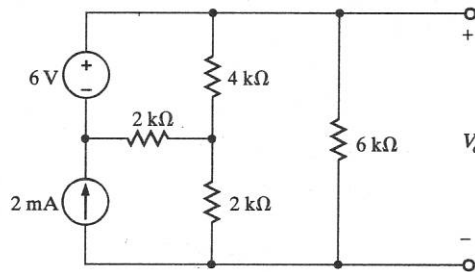


Figure P3.46

Problem 6: Use both nodal analysis and mesh analysis to find V_o in the circuit in Fig. P3.51.

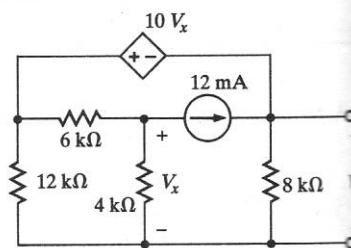


Figure P3.51