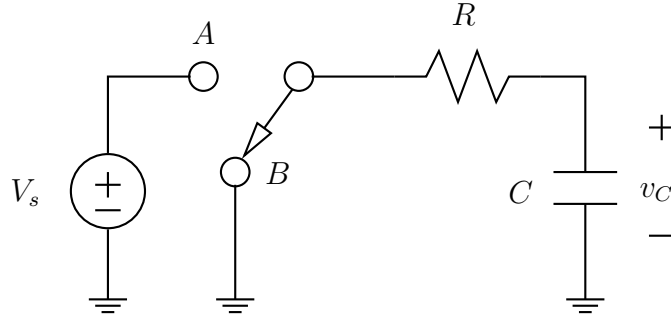


EEE 33 first semester AY2011-2012 : Homework 3

1. The switch in the circuit below has been at position  $B$  for a long time.

At time  $t = 0, 2T, 4T, \dots$ , the switch moves to position  $A$  where  $T$  is some time interval.

At time  $t = T, 3T, 5T, \dots$ , the switch moves to position  $B$ .



- Determine and plot  $v_C(t)$  for  $0 < t \leq T$ . What are  $v_C(T^-)$  and  $v_C(T^+)$ ?
- Determine and plot  $v_C(t)$  for  $T < t \leq 2T$ . What are  $v_C(2T^-)$  and  $v_C(2T^+)$ ?
- Determine  $v_C(3T)$ ,  $v_C(4T)$ , and  $v_C(5T)$ .
- Determine a general form for  $v_C(kT)$  where  $k$  is an odd integer.


2. Given that for  $|x| < 1$ ,

$$\frac{1}{1-x} = 1 + x + x^2 + x^3 + \dots$$

- For large  $k$  in part 1(d), use the above identity to write a simple expression for  $v_C(kT)$ .
- If  $RC = 100T$ , show that  $v_C(kT) \approx V_s/2$  for large  $k$ .

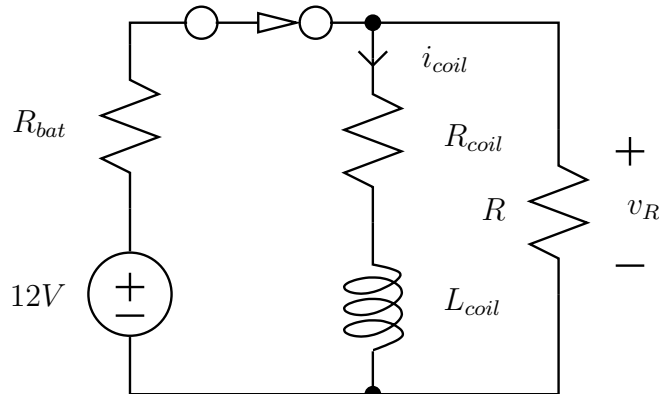3. The switch in the circuit below has been closed for a long time.

At time  $t = 0$ , the switch is opened. Given that  $R_{bat} = 4 \Omega$ ,  $R_{coil} = 2 \Omega$ , and  $R = 10 k\Omega$ ,



- What are  $i_{coil}(0^-)$ ,  $i_{coil}(0^+)$ ,  $v_R(0^-)$  and  $v_R(0^+)$ ?
- Determine  $i_{coil}(t)$  and  $v_R(t)$  for  $t \geq 0$ .
- Plot  $i_{coil}(t)$  and  $v_R(t)$  for  $t \geq 0$ .

4. For problem 3, determine the value of  $L_{coil}$  such that  $v_R(1 \text{ ms}) = 0.5v_R(0^+)$ . Show your solution. Plot  $v_R(t)$ .