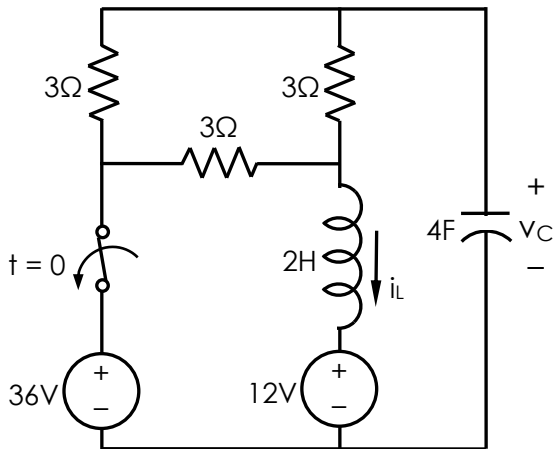


EEE 33 1st Semester AY 2011-2012: Homework 4

Page 1 of 2


Problem 1: Evaluating Initial Conditions

Solve for i_L , i_L' , v_C , and v_C' at $t=0^+$.



Problem 2: The Steady-State Response

Find the steady-state response of $i(t)$ for $t>0$.

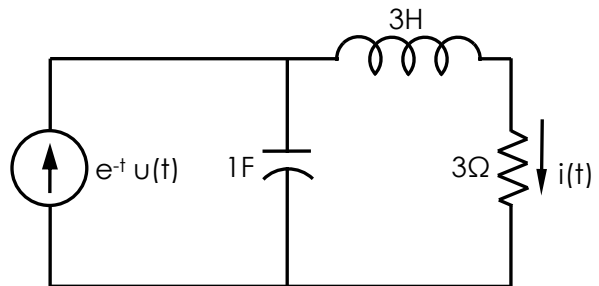


Problem 3: Solving the Differential Equation

The voltage across the inductor L_1 is given by:

$$\frac{d^3 v}{dt^3} + 4 \frac{d^2 v}{dt^2} + 5 \frac{dv}{dt} + 2v = 0$$

Find $i_R(t)$ for $t > 0$ if $i_R(0^+) = 0$, $i_R'(0^+) = 0$, and $i_R''(0^+) = -2 \text{ A/s}^2$.

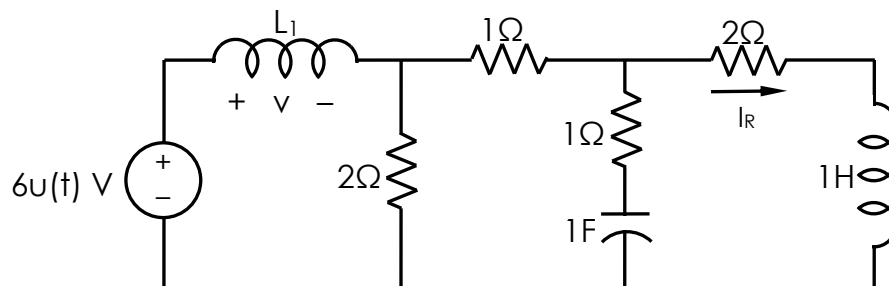

Problem 4: Second-Order Transients

1. Formulate the state equations describing the circuit for $t > 0$.
2. Solve for $i_L(0^+)$, $v_C(0^+)$, $i_L'(0^+)$, and $v_C'(0^+)$.
3. Solve for $v_C(t)$ for $t > 0$.
4. Solve for $i_R(t)$ at $t = 0.2\text{s}$.

