

EEE 33 1st Semester AY 2011-2012: Homework 6

Problem 1 – Complex Power

Three parallel loads are supplied by a 440V source. Load A draws 10kVA at 0.8 pf lead, load B draws 15kW at 0.5 pf lag, and load C draws 5kW at unity pf. Determine the following:

- the real power, reactive power, and apparent power drawn by each load
- the real power, reactive power, and apparent power supplied by the 440V line
- the current drawn by the combined load
- the equivalent power factor of the combined load
- the value of the capacitance that must be connected across the line so that the source will operate at unity pf at 60 Hz
- the value of the capacitance in e if the source should operate at 0.9 pf lead instead

Problem 2 – Phasor Diagrams

The phasor quantities in the table below describe all the phasor voltages and currents of an RLC circuit supplied with a sinusoidal voltage source V_s .

PHASOR QUANTITY	MAGNITUDE (V OR A)	ANGLE (DEGREES)
I_1	3	90
V_{1a}	12	90
V_{1b}	6	180
V_{1c}	15	0
V_2	15	53.1301
I_{2a}	5	-36.8699
I_{2b}	1	53.1301
I_s	4.669	9.8658
V_{RS}	46.6905	9.8658
V_s	58.5235	19.9831

- Draw the phasor diagram. Label the magnitudes and phase angles in the diagram.
- From the phasor relationships, determine the values and connections of the different circuit components.

Problem 3 – Balanced Three-Phase Systems

A three phase Y-connected load is drawing 20kW at 0.8 pf lag from a Δ -connected generator through feeders having a resistance of 1.0Ω and inductive reactance of 1.0Ω each. If the line to line voltage at the load is 230V, compute the following:

- the magnitude of the load phase voltages
- the magnitude of the line current
- the magnitude of the generator line to line voltages
- the magnitude of the generator phase currents
- the operating power factor of the generator

Problem 4 – Single Phase Transformers

A single phase load is supplied through a 35kV feeder* with an input impedance of $115 + j380 \Omega$ and a 35kV : 2.4kV non-ideal transformer whose equivalent impedance is $0.2 + j1.21 \Omega$ referred to its low-voltage side. If the load is drawing 180kW at 0.87 pf lead at 2.32kV, determine the following:

- the single phase circuit diagram
- the voltage at the high voltage terminals of the transformer
- the voltage at the sending end of the feeder
- the P and Q at the sending end of the feeder

*A 35 kV feeder refers to a transmission line that transmits power at the 35 kV range. The voltages at the sending and receiving end are not necessarily equal to 35 kV, but close to it.

Problem 5 – Three Phase Transformers

Three identical single phase transformers with nameplate ratings of 10kVA 440V : 110V each are connected together to form a three-phase transformer bank. The primary windings of the transformers are connected in Y while the secondary windings are connected in Δ . If the transformer primary is supplied by a 700 V source, determine the following:

- the schematic diagram of the primary and secondary windings of the 3-phase transformer: label the phases and indicate the polarity marks if V_{an} lags V_{AN} by 30° , V_{bn} lags V_{BN} by 30° , and V_{cn} lags V_{CN} by 30° **. Assume an acb phase sequence.
- the nominal line to line voltage at the secondary
- the maximum real power that can be supplied to a 0.866 pf lag load at the secondary
- the maximum secondary current that the transformer can supply to a load
- the line current drawn at the transformer primary if a Y-connected three phase load with a per phase impedance of $2 + j2 \Omega$ is connected at the transformer secondary

**Note that the capital letters represent the primary phases whereas small letters represent the secondary phases. Also note that the transformer can be connected in such a way that the phase to neutral voltages are displaced by an angle other than 30° .

Problem 6 – Superposition

A triangular voltage waveform can be approximated by a summation of sinusoids of specific amplitudes and frequencies, i.e.

$$V_s(t) = \frac{8A}{\pi^2} \sum_{n=\text{odd}}^{\infty} \frac{(-1)^{(n-1)/2}}{n^2} \sin\left(\frac{n\pi t}{T}\right) \text{ Volts}$$

where $n \in \{1, 3, 5, 7, 9, \dots\}$, A is the amplitude, and T is the period of the waveform.

Using $n \in \{1, 3, 5\}$, $A = 1$, $T = 2$, and the circuit shown below, determine the following:

- the voltage supplied by the source as function of t
- the sketch of the source voltage for $0 < t < 10$ (you may use a plotting software for this)
- the voltage across Z_2 as function of t
- the current through Z_2 as function of t

