

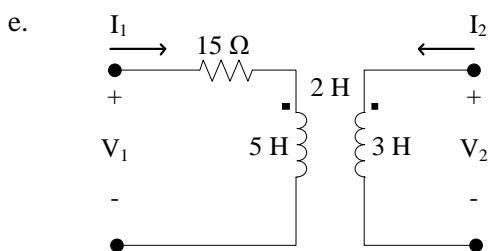
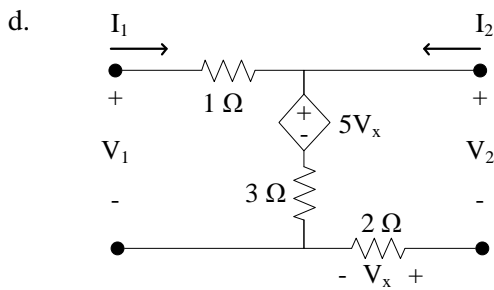
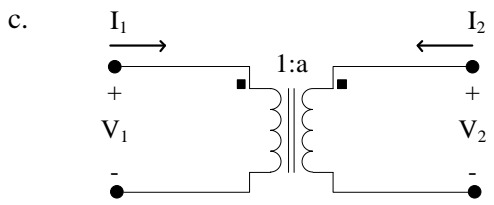
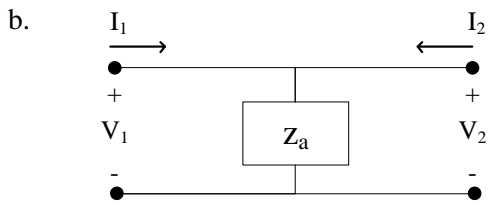


EEE 33 1s1112: Homework 8

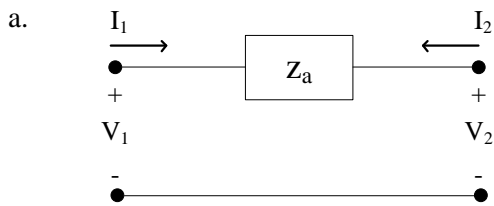1. Determine the **z**, **y**, **h** and **t** parameters for the following networks:



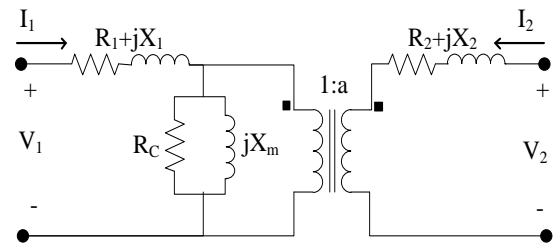2. The next figure shows the model for a non-ideal transformer. The model contains resistances, inductances, and an ideal transformer. Find the model's **t** parameters by
 a. using circuit analysis.
 b. using the **t** parameters derived in (1a), (1b), and (1c).





$$\begin{aligned}
 R_1 &= 0.650 \, \Omega & R_c &= 30.86 \, \text{k}\Omega \\
 X_1 &= 8.40 \, \Omega & X_m &= 4.46 \, \text{k}\Omega \\
 R_2 &= 0.00650 \, \Omega & a &= 0.1 \\
 X_2 &= 0.00840 \, \Omega & &
 \end{aligned}$$


3. The **z** parameters for networks A and B are

$$\mathbf{Z}_A = \begin{bmatrix} Z_{A,11} & Z_{A,12} \\ Z_{A,21} & Z_{A,22} \end{bmatrix}, \quad \mathbf{Z}_B = \begin{bmatrix} Z_{B,11} & Z_{B,12} \\ Z_{B,21} & Z_{B,22} \end{bmatrix}$$

Determine the **z** parameters of

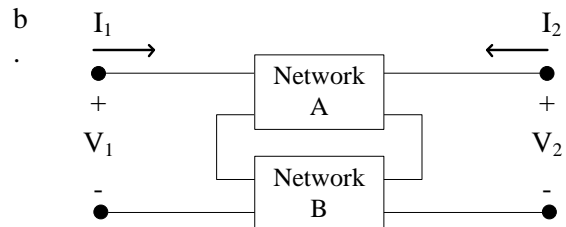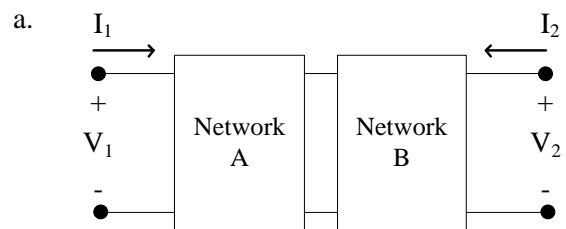

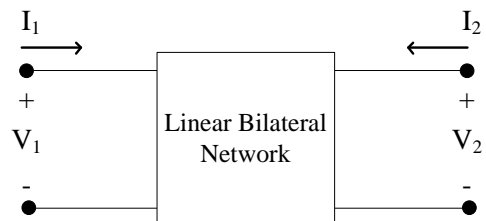4. Determine the **z**, **y**, **h**, and **t** parameters of the network from the tabulated data.



V_1	I_1	V_2	I_2
50 V	4 A	60 V	-6 A
180 V	32 A	80 V	-28 A