

Chapter 10

Two – Port Networks


EEE 33

1st Semester 2005-2006




Department of Electrical and Electronics Engineering


University of the Philippines - Diliman

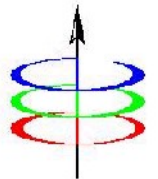


Definition of Two-Port Networks

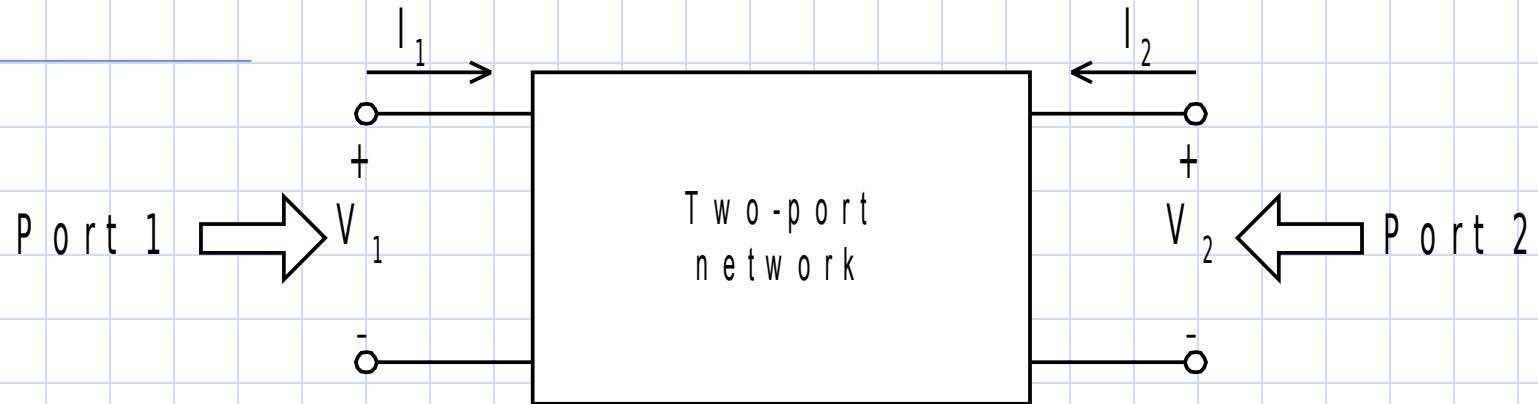

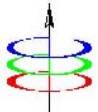
- In general, we describe a **two-port network** as a network consisting of R, L, and C elements, op-amps, transformers, and dependent sources, but no independent sources.
- Only two of the four variables are independent, and the specification of any two of them determines the remaining two.




Examples of Two-Port Networks

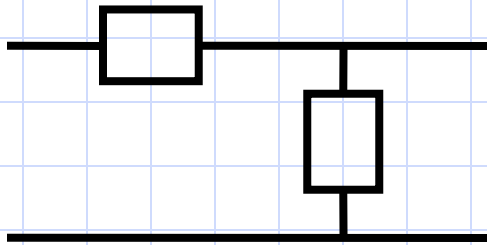


L - network

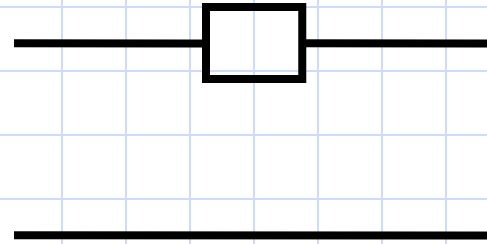


Series

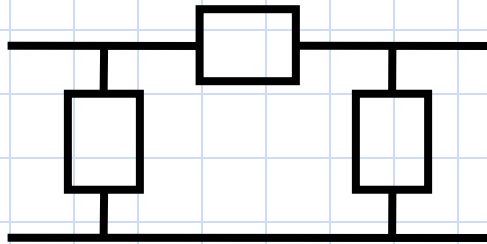


Pi network

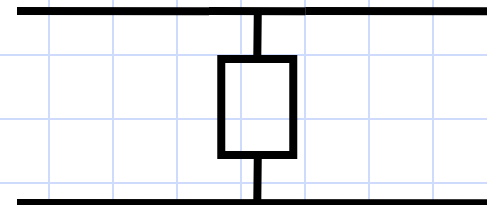


Shunt

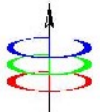


Examples of Two-Port Networks

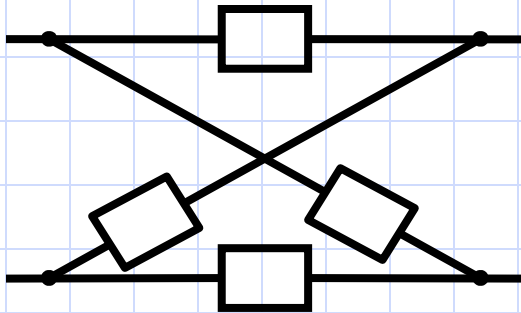


Lattice

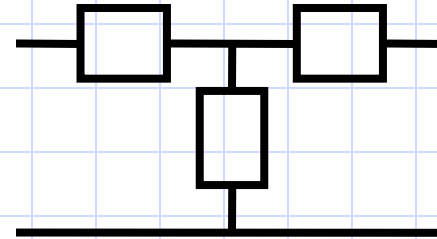


T network

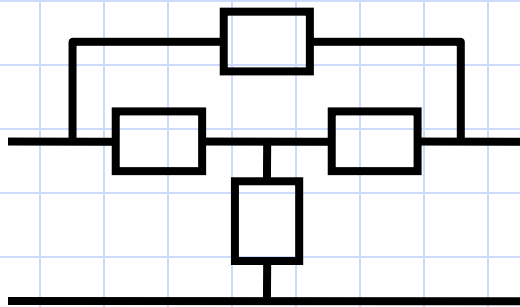


Bridged T

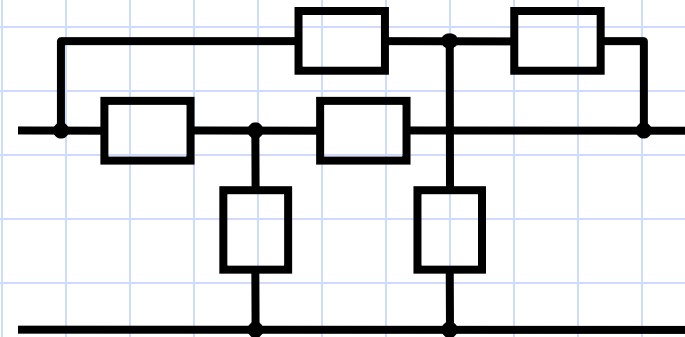

Twin T

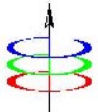


Two-Port Network Parameters

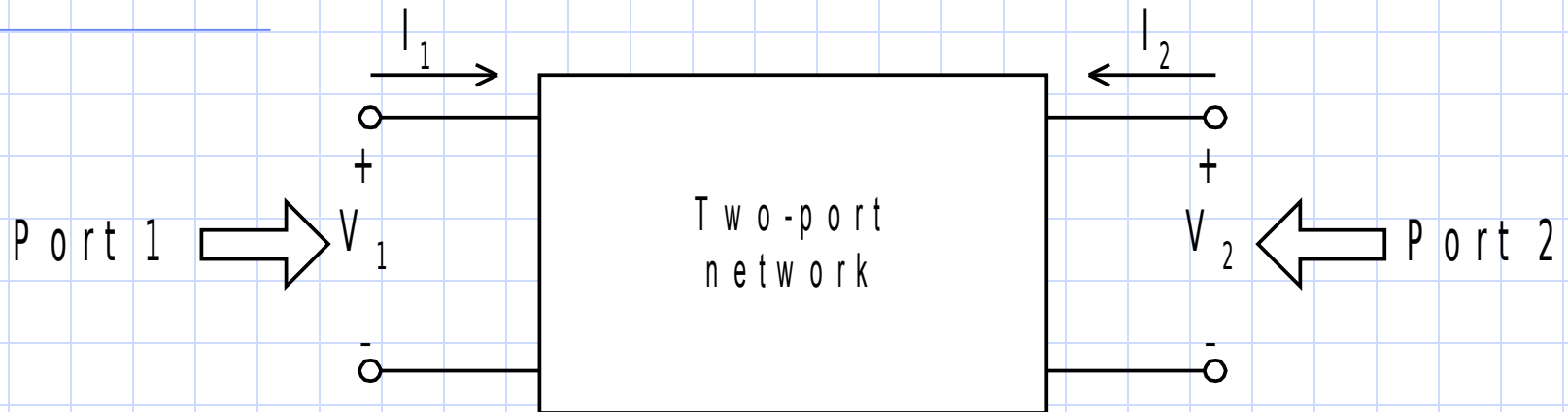


Parameters of the two-port completely describe its behavior in terms of the voltage and current at each port.

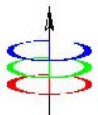- ◆ Permits us to describe its operation when it is connected to a larger network.
- ◆ Important in modeling electronic devices and system components.



Two-Port Parameters

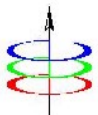- ◆ Admittance Parameters (y_{jk})
- ◆ Impedance Parameters (z_{jk})
- ◆ Hybrid Parameters (h_{jk})
- ◆ Transmission Parameters (t_{jk})




Admittance Parameters

- V_1 and V_2 are the independent variables
- Express I_1 and I_2 in terms of V_1 and V_2

$$I_1 = y_{11}V_1 + y_{12}V_2$$

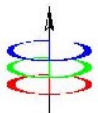
- The coefficients y_{jk} are also called the **short-circuit admittance parameters** or the **y-parameters**
- The coefficients y_{jk} are dimensionally admittance



Getting the Short-Circuit Admittance Parameters (y-parameters)


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

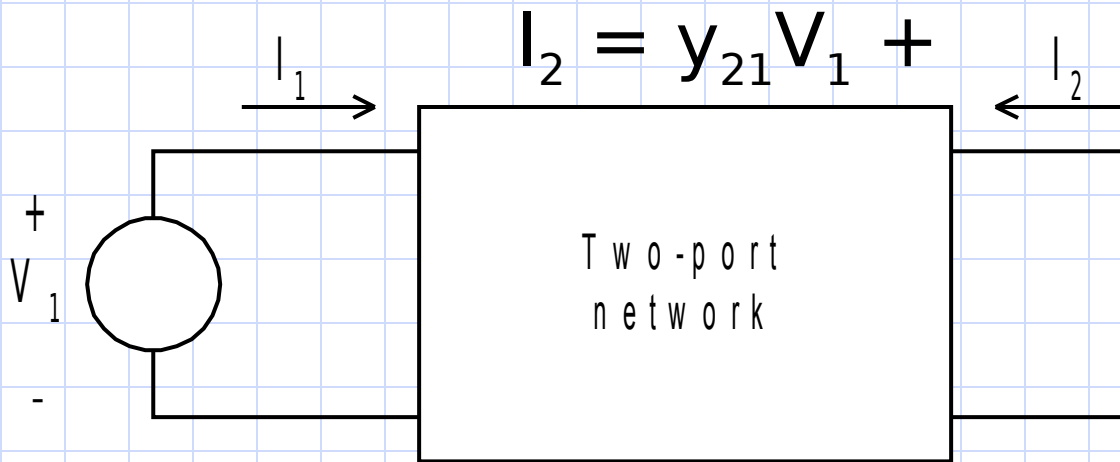

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$


$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

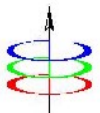

Getting the Short-Circuit Admittance Parameters (y-parameters)


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

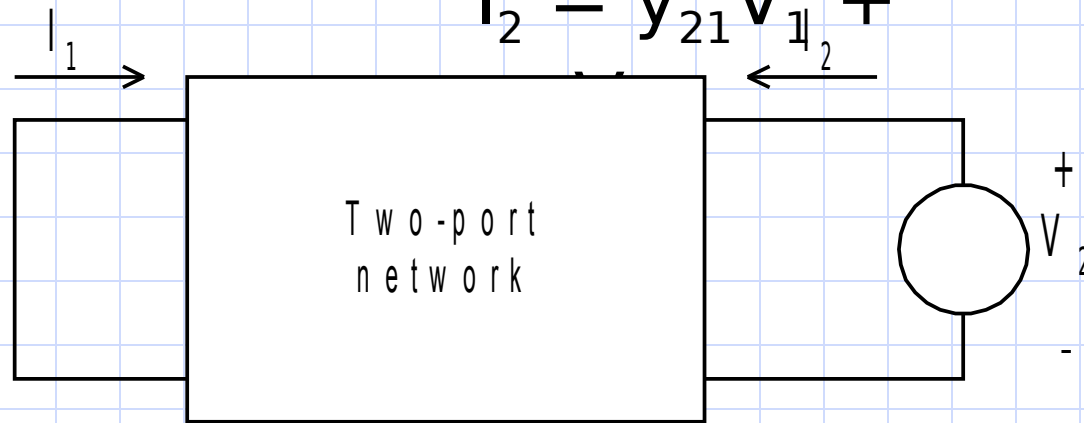


$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

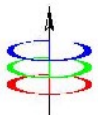


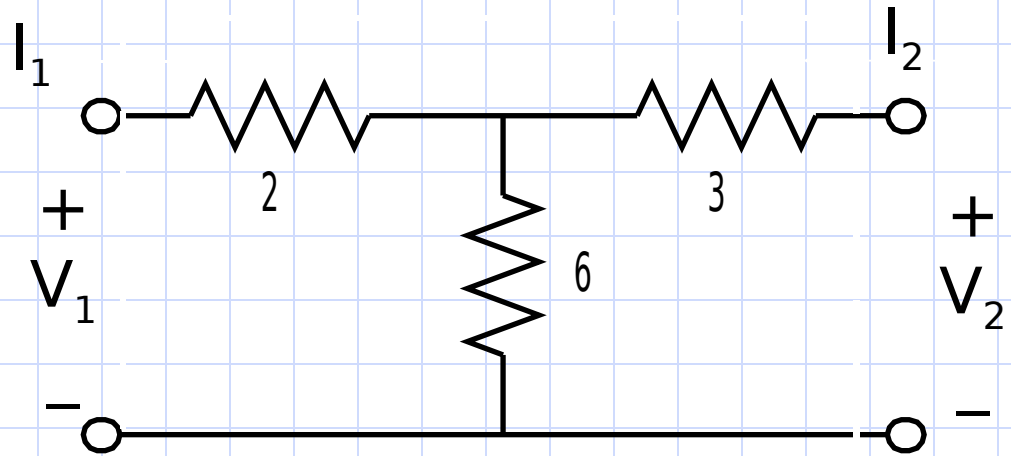Example: Find the Y-parameters of the two-port network on the right.



Get the y-parameters one by one.


y_{11} :

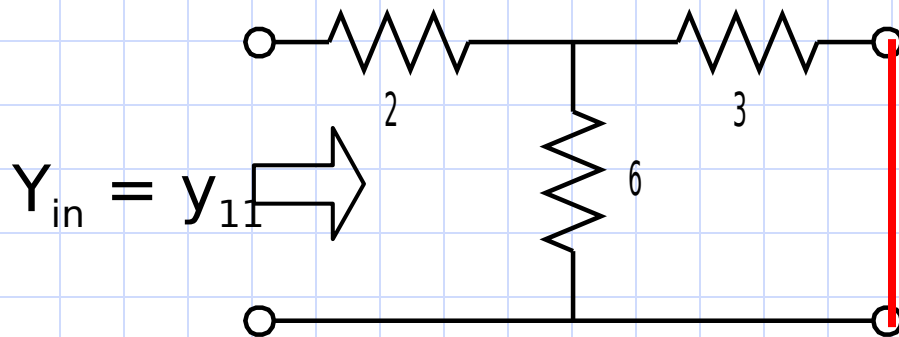


$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$y_{11} = \frac{1}{2 + \frac{3}{6}}$$

$$= \frac{1}{4}$$

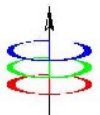


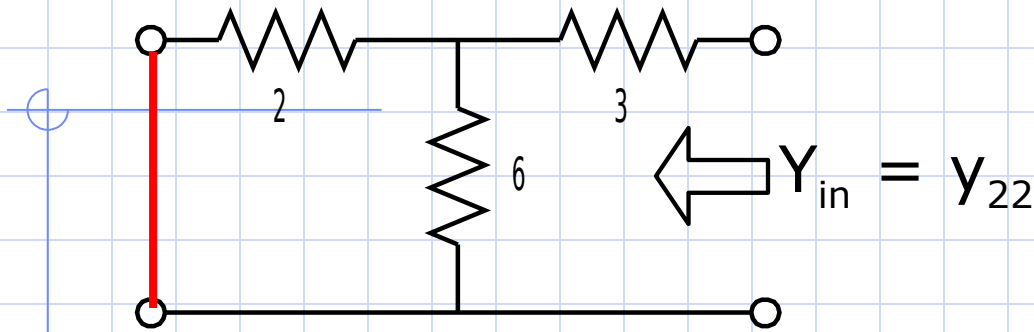Y_{22} 

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$y_{22} = \frac{1}{3 + 2//6} \text{ } \overline{\text{U}}$$


$$= \frac{2}{9}$$

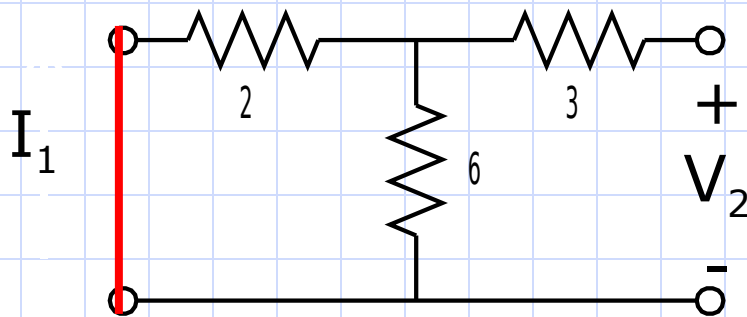 Y_{12} 


$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{12} = \frac{I_1}{V_2} = \frac{-\frac{3}{4} V_2 Y_{22}}{V_2}$$
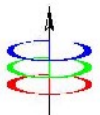
$$= -\frac{3}{4} Y_{22} = -1/6 \text{ } \overline{\text{U}}$$




Y_{21}

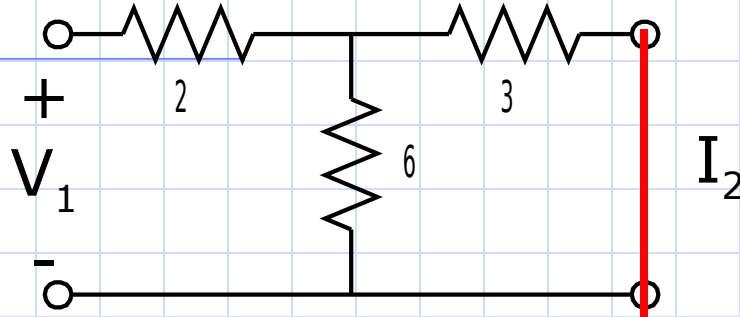


$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{21} = I_2 / V_1 = -\frac{2}{3} V_1 y_{11} / V_1$$
$$= -2/3 y_{11} = -1/6 \text{ } \overline{\Omega}$$

Thus, we get

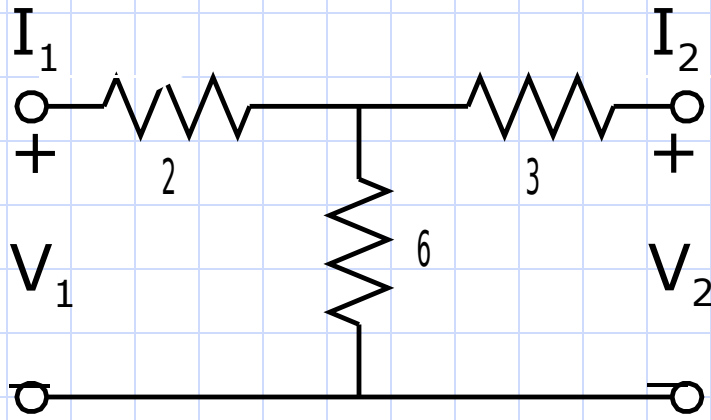

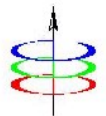
$$I_1 = 1/4 V_1 - 1/6 V_2$$
$$I_2 = -1/6 V_1 + 2/9 V_2$$



Or in matrix form,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$
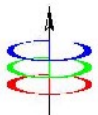
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{4} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{2}{9} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$




Impedance Parameters

- I_1 and I_2 are the independent variables
- Express V_1 and V_2 in terms of I_1 and I_2

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

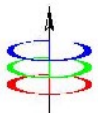- Also known as the **open-circuit impedance parameters** or the **z-parameters**
- The coefficients are dimensionally impedance




Impedance Parameters


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \qquad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \qquad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

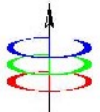

Example: Find the Z-parameters of the two-port network on the right.

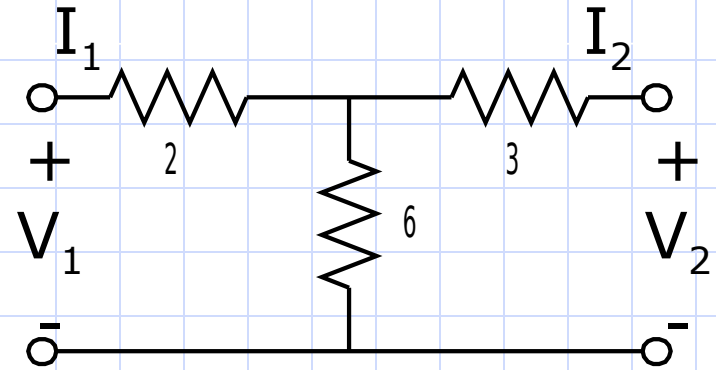

Method 1: Using the definitions,

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{11} = 2 + 6 = 8 \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$


$$z_{21} = 6 \Omega$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$


$$z_{12} = 3 + 6 = 9 \Omega$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$z_{22} = 6 \Omega$$

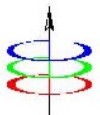

Method 2: By writing loop equations,

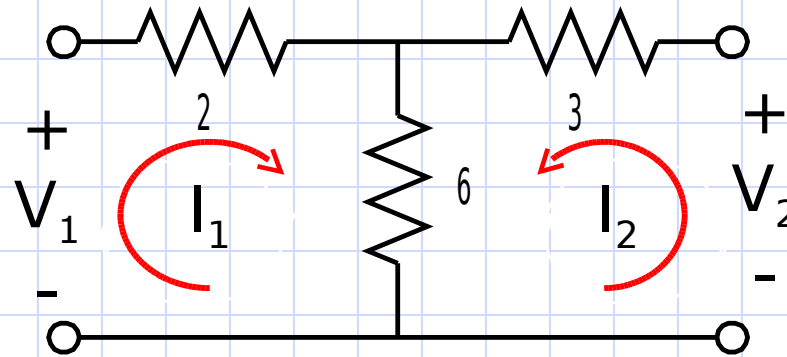


$$V_1 = 2I_1 + 6(I_1 + I_2) = 8I_1 + 6I_2$$

$$V_2 = 3I_2 + 6(I_1 + I_2) = 6I_1 + 9I_2$$

Therefore,
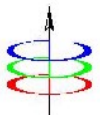
$$z_{11} = 8, z_{12} = 6, z_{21} = 6 \text{ and } z_{22} = 9$$



Relationship Between Y- and Z-parameters

Let $\mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$ and $\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$


We know $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$ $\mathbf{I} = \mathbf{YV}$

Solving for V: $\mathbf{V} = \mathbf{Y}^{-1}\mathbf{I}$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \mathbf{V} = \mathbf{ZI}$$

Therefore,
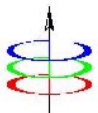
$$\mathbf{Z} = \mathbf{Y}^{-1} \text{ or } \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$$





Hybrid Parameters

- Also known as **H-parameters**
- Often used to model the small signal behavior of bipolar junction transistors

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

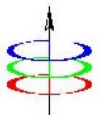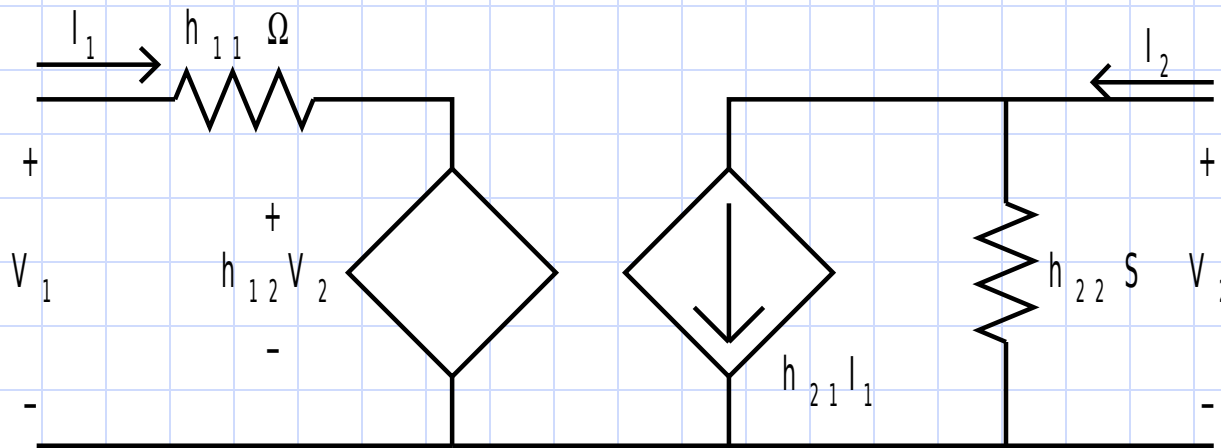

Getting the H-parameters

$$V_1 = h_{11}I_1 + h_{12}V_2$$


$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

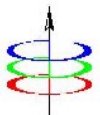

Converting Z- to H-parameters

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad V_2 = z_{21}I_1 + z_{22}I_2$$

Express V_1 and I_2 with in terms of V_2 and I_1

$$I_2 = -\frac{z_{21}}{z_{22}}I_1 + \frac{1}{z_{22}}V_2$$

$$h_{11} = z_{11} - \frac{z_{12}z_{21}}{z_{22}}$$


$$V_1 = z_{11}I_1 + z_{12}\left(-\frac{z_{21}}{z_{22}}I_1 + \frac{1}{z_{22}}V_2\right) \quad \rightarrow$$

$$= \left(z_{11} - z_{12}\frac{z_{21}}{z_{22}}\right)I_1 + \frac{z_{12}}{z_{22}}V_2$$

$$h_{12} = \frac{z_{12}}{z_{22}}$$

$$h_{21} = -\frac{z_{21}}{z_{22}}$$

$$h_{22} = \frac{1}{z_{22}}$$

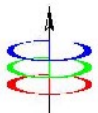

Inverse Hybrid Parameters

- Also known as **G-parameters**

$$I_1 = g_{11}V_1 + g_{12}I_2$$


$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

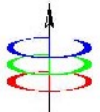


Transmission Parameters

- The **transmission parameters** relate the voltage and current at one port of the network with those of the other end.

$$\begin{array}{l} V_1 = t_{11}V_2 - t_{12}I_2 \\ I_1 = t_{21}V_2 - t_{22}I_2 \end{array} \quad \text{or} \quad \begin{array}{l} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{array}$$

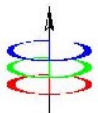- The transmission parameters are also known as the **chain parameters, general circuit parameters, or ABCD parameters**



Transmission Parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$


$$\frac{1}{A} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad -\frac{1}{B} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad \frac{1}{C} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad -\frac{1}{D} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

1/A - open-circuit voltage gain


-1/B - short-circuit transfer admittance

1/C - open-circuit transfer impedance

-1/D - short-circuit current gain

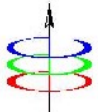

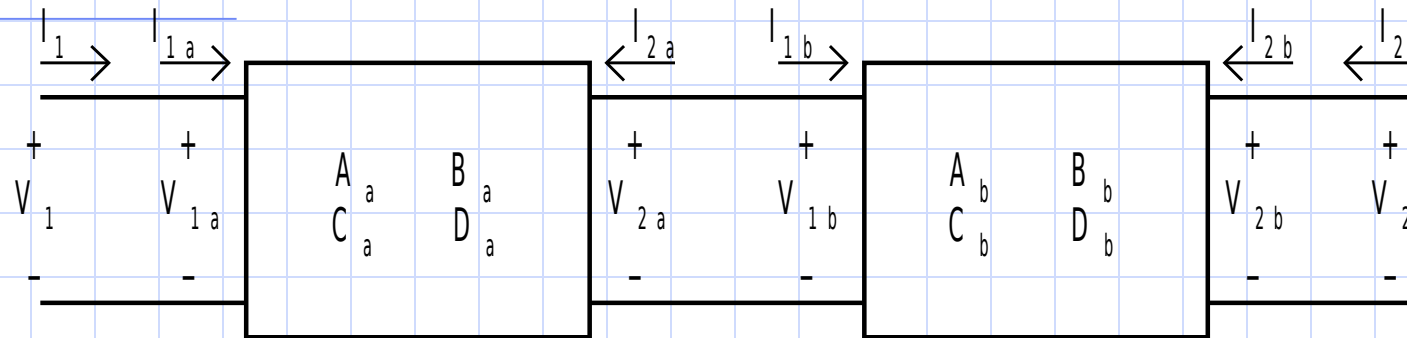The t-parameters are useful in describing two-port networks which are connected in cascade.




$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$\text{but } \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} = \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} \text{ so } \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

Therefore, in
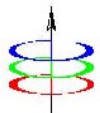
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}, \quad \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$



Inverse Transmission Parameters

- Also known as **ABCD'** parameters

$$V_2 = A'V_1 - B'I_1$$

$$I_2 = C'V_1 - D'I_1$$

- For passive networks,

$$AD - BC = A'D' - B'C' = 1$$

